
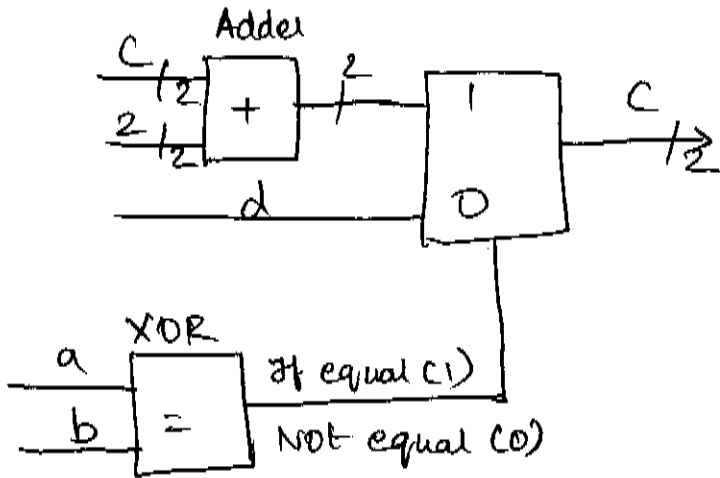


Homework 6

3a)

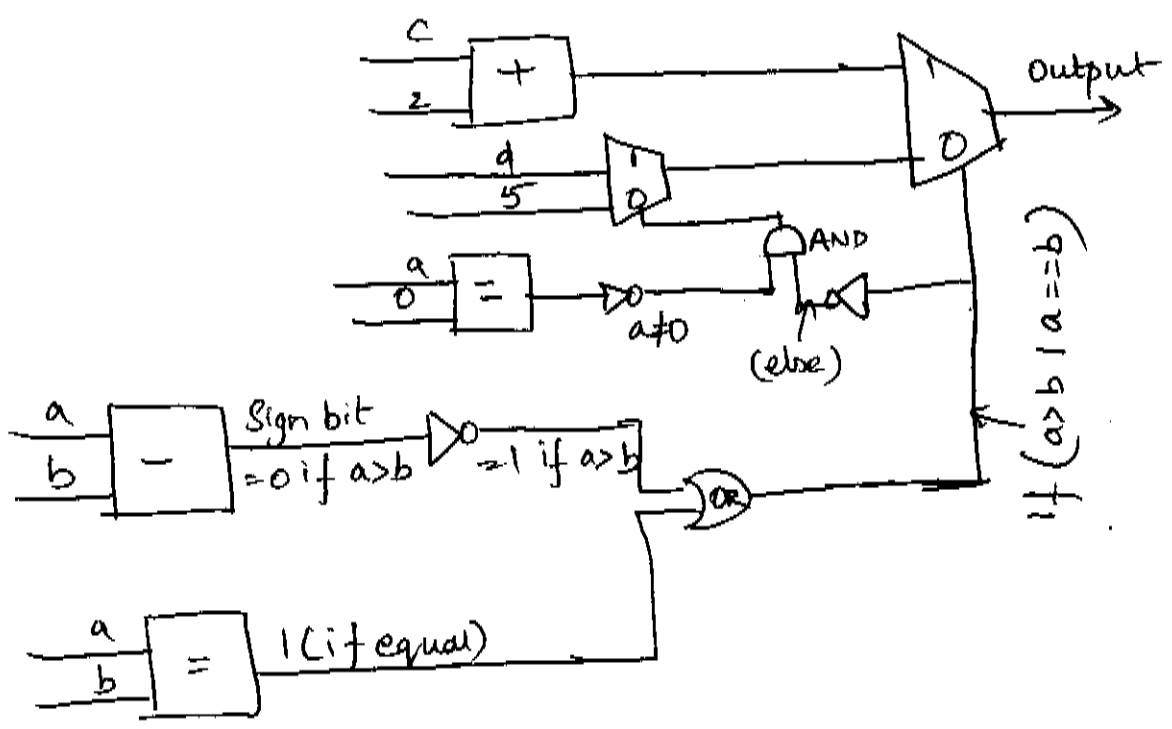


4)



5a) State Transition Diagram

Regular expressions:-

:"0*1 + 0c(10)*"

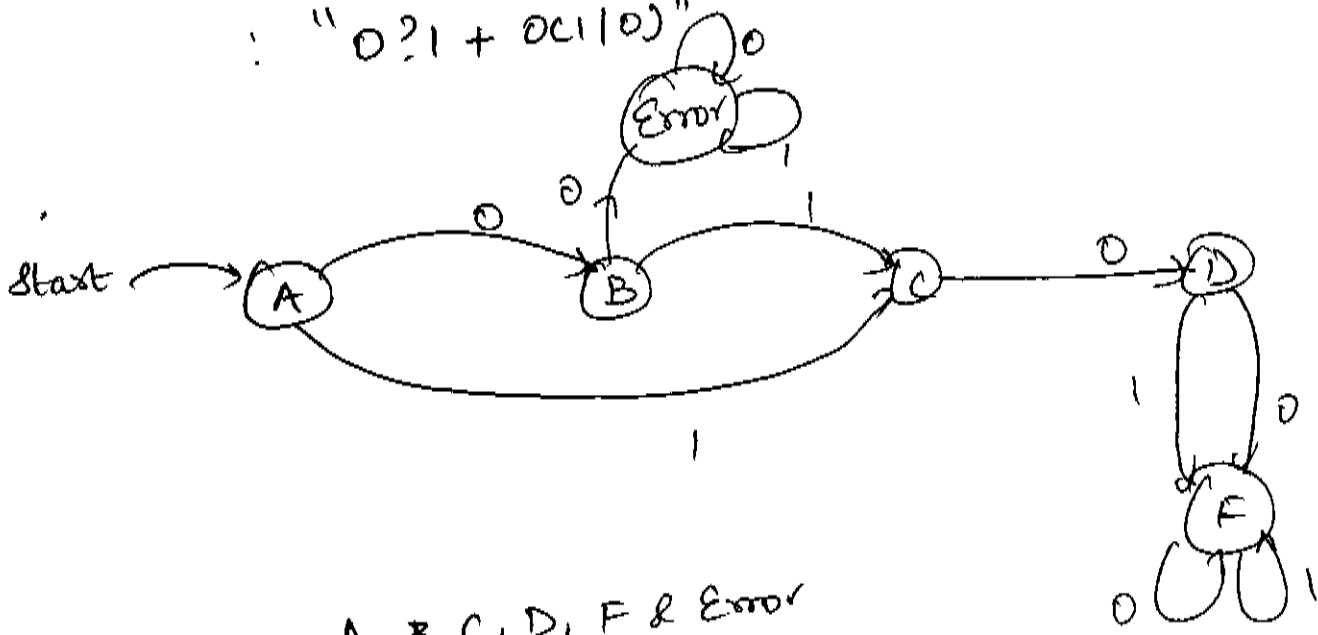

States are A, B, C, D, E & Error

Binary value	Current state	Inputs		Accepted	Error
		0	1		
0000	A	B	C		
0010	B	E	C		
0100	C	D	C		
0110	D	F	F		
1000	E	E	E		1
1010	F	F	F	1	

There are 6 states, we need a minimum of 3 bits to represent the states
 let $q_2 = a$, $q_1 = b$, $q_0 = c$ & Input = d

State Table

Current State: Input	a				a _{next}	a _{next}			Output	
	a ₂	a ₁	a ₀	Input		a ₂	a ₁	a ₀	f	e
A: 0	0	0	0	0	B	0	0	1		
A: 1	0	0	0	1	C	0	1	0		
B: 0	0	0	1	0	E	1	0	0		
B: 1	0	0	1	1	C	0	1	0		
C: 0	0	1	0	0	D	0	1	1		
C: 1	0	1	0	1	C	0	1	0		
D: 0	0	1	1	0	F	1	0	1		
D: 1	0	1	1	1	E	1	0	1		
E: 0	1	0	0	0	E	1	0	0		
E: 1	1	0	0	1	E	1	0	0		
F: 0	1	0	1	0	F	1	0	1	1	
F: 1	1	0	1	1	F	1	0	1	1	
G: 0	1	1	0	0	X	X	X	X		
G: 1	1	1	0	1	X	X	X	X		
H: 0	1	1	1	0	X	X	X	X		
H: 1	1	1	1	1	X	X	X	X		

Don't care states

a_2 K Map

	$\bar{c}\bar{d}$	$\bar{c}d$	cd	$c\bar{d}$
$\bar{a}\bar{b}$				1
$\bar{a}b$			1	1
ab	X	X	X	X
$a\bar{b}$	1	1	1	1

$$a_2 = a + bc + c\bar{d}$$

a_1 K Map

	$\bar{c}\bar{d}$	$\bar{c}d$	cd	$c\bar{d}$
$\bar{a}\bar{b}$		1	1	
$\bar{a}b$	1	1		
ab	X	X	X	X
$a\bar{b}$				

$$a_1 = b\bar{c} + \bar{a}\bar{b}d$$

f K Map (Accepted State)

	$\bar{c}\bar{d}$	$\bar{c}d$	cd	$c\bar{d}$
$\bar{a}\bar{b}$				
$\bar{a}b$				
ab	X	X	X	X
$a\bar{b}$			1	1

$$f = ac$$

a_2 K Map

	$\bar{c}\bar{d}$	$\bar{c}d$	cd	$c\bar{d}$
$\bar{a}\bar{b}$	1			
$\bar{a}b$	1		1	1
ab	X	X	X	X
$a\bar{b}$			1	1

$$a_2 = \bar{a}\bar{c}\bar{d} + bc + ac$$

Error K-Map (Error Condition)

	$\bar{c}\bar{d}$	$\bar{c}d$	cd	$c\bar{d}$
$\bar{a}\bar{b}$				
$\bar{a}b$				
ab	X	X	X	X
$a\bar{b}$	1	1		

$$\text{Error} = a\bar{c}$$