
 


1(a) (5 points) Fill in the truth table for the following logic and assume zero gate delay.

1(b) (20 points) Now fill in the timing diagram where each time step is 1 nanosecond and include the triggering lines using following gate delays: AND is 1 nanosecond delay, OR has 1 nanosecond delay and the NAND gate has 2 ns delay.


a	b	c	g	h	f
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	0	1	1
0	1	1	0	1	1
1	0	0	0	0	1
1	0	1	0	1	1
1	1	0	1	1	0
1	1	1	1	1	0

 


$\square$  = unknown

1(c) (10 points) Redraw the logic diagram of problem 1 using only 2-input NOR gates. Do not use NANDs, NOTs, ANDs, ORs, XORs, XNORs, etc.

Step 1

 

Step 2

 


Also acceptable




Step 2



Step 3

 

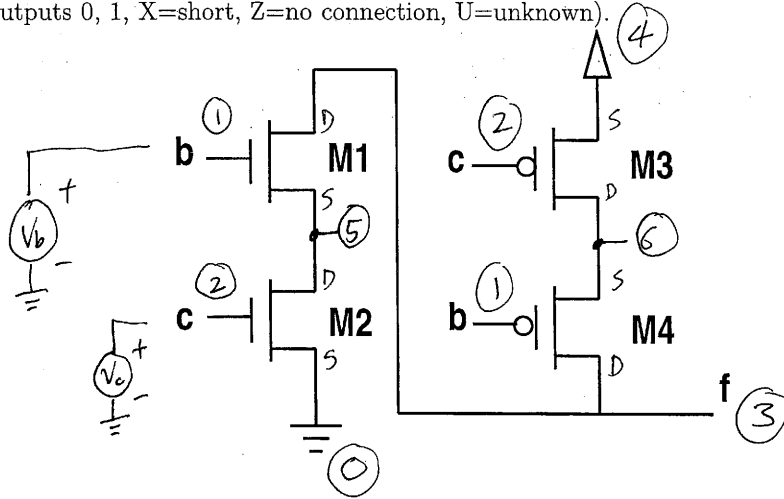2(a) (15 points) Fill in the following function table of the CMOS circuit below and label all the CMOS drains ( $D$ ) and sources ( $S$ ) on the circuit. For the CMOS circuit, assume  $V_{dd} = 1$  Volt and a  $V_t$ , threshold voltage of zero. (note: possible outputs 0, 1, X=short, Z=no connection, U=unknown).




Inputs		M1				M2				M3				M4				f
b	c	$V_g$	$V_s$	on/off	$V_d$	$V_g$	$V_s$	on/off	$V_d$	$V_g$	$V_s$	on/off	$V_d$	$V_g$	$V_s$	on/off	$V_d$	f
0	0	0	Z	off	Z	0	0	off	Z	0	1	on	1	0	1	on	1	1
0	1	0	0	off	Z	1	0	on	0	1	1	off	Z	0	Z	off	Z	Z
1	0	1	Z	off	Z	0	0	off	Z	0	1	on	1	1	1	off	Z	Z
1	1	1	0	on	0	1	0	on	0	1	1	off	Z	1	Z	off	Z	0

2(b) (20 points) Fill in the missing SPICE parameters below for the above CMOS circuit, Using a rise and fall time of 0.2 nanoseconds and the input signals from timing diagram of problem 1.


```

*
  D   G   Src   Sub
M1   3   1   5   0   T1   W=3.6U L=1.2U
M2   5   2   0   0   T1   W=3.6U L=1.2U
M3   6   2   4   4   W1   W=3.6U L=1.2U
M4   3   1   6   4   W1   W=3.6U L=1.2U
*
Vdd  4   0   DC=1.0
*
Vb   1   0   PWL( ON 1 2N 1 2.2N 0 5N 0 5.2N 1 9N 1 )
*
Vc   2   0   PWL( ON 1 1N 1 1.2N 0 3N 0 3.2N 1 9N 1 )
*
.TRAN 0.1N 9N
*
.MODEL T1 NMOS LEVEL=1 KP=48E-6 LAMBDA=0.032 VTO=0.88 GAMMA=0.66 PHI=0.7
.MODEL W1 PMOS LEVEL=1 KP=16E-6 LAMBDA=0.044 VTO=-0.85 GAMMA=0.69 PHI=0.7
.END
  
```

 3. (10 points) Fill in the timing diagram for the following circuit using 1 ns delay for the NAND gate.



4 For the following circuit:

 

4(a) (5 points) Give the Boolean expression for

$$f(a, b, c, d) = \overline{(a \cdot b)} + (c \oplus d)$$

4(b) (5 points) Give the VHDL in one statement for

$$f <= (a \text{ NAND } b) \text{ NOR } (c \text{ XOR } d)$$

4(c) (5 points) Give the C++/JAVA using "bitwise" operators in one statement for

$$f = \sim(\sim(a \& b)) | (c \wedge d)$$

4(d) (5 points) Give the C++/JAVA using **only** "logical" operators in one statement for

$$f = !(! (a \&\& b)) || ((! c \&\& d) || (c \&\& ! d))$$

(X1) (Extra Credit, 5 points): Write the Boolean expression for a Coffee machine which outputs coffee (f) whenever 30 cents or more is deposited. The machine can only accept only one nickel, one dime and one quarter. Assume the variables, a is nickel deposited, b is a dime deposited, c is a quarter deposited.

$$f = ca + cb = c(a + b) \quad f = b \cdot c + a \cdot c + abc$$

$$= c(b + c) + abc$$