

# EECS 322: Computer Architecture



**Single-cycle  
Multi-cycle FSM controller  
Multi-cycle microcontroller**




# MIPS instruction formats




## Arithmetic

**add \$rd,\$rs,\$rt**

 

 
## Data Transfer

**lw \$rd,offset(\$rs)**  
**sw \$rd,offset(\$rs)**




## Conditional branch

**beq \$rd,\$rs,raddr**

 


## Unconditional jump

**j addr**

 
 
# Single Cycle Implementation

- Calculate instruction cycle time assuming negligible delays except:
  - memory (2ns), ALU and adders (2ns), register file access (1ns)



Single Cycle = 2 adders + 1 ALU

# Single/Multi-Clock Comparison



- add** = 6ns = Fetch(2ns)+RegR(1ns)+ALU(2ns)+RegW(2ns)
- lw** = 8ns = Fetch(2ns)+RegR(1ns)+ALU(2ns)+MemR(2ns)+RegW(2ns)
- sw** = 7ns = Fetch(2ns)+RegR(1ns)+ALU(2ns)+MemW(2ns)
- beq** = 5ns = Fetch(2ns)+RegR(1ns)+ALU(2ns)
- j** = 2ns = Fetch(2ns)

$$\frac{\text{CPU single-cycleclock}}{\text{CPU multi-cycleclock}} = \frac{8ns}{6.3ns} = 1.27 \text{ times faster}$$

**Architectural improved performance without speeding up the clock!**

# Some Design Trade-offs



## High level design techniques

**Algorithms:** change instruction usage

$$\text{minimize } \sum n_{\text{instruction}} * t_{\text{instruction}}$$

**Architecture:** Datapath, FSM, Microprogramming

adders: ripple versus carry lookahead

multiplier types, ...

## Lower level design techniques (closer to physical design)

**clocking:** single versus multi clock

**technology:** layout tools: better place and route

process technology: 0.5 micron to .18 micron

# Single-cycle problems



- Single Cycle Problems:
  - what if we had a more complicated instruction like floating point? (fadd = 30ns, fmul=100ns)
  - wasteful of area (2 adders + 1 ALU)
- One Solution:
  - use a “smaller” cycle time (**if the technology can do it**)
  - have different instructions take different numbers of cycles
  - a “multicycle” datapath (1 ALU)
- Multi-cycle approach
  - We will be reusing functional units:
    - ALU used to increment PC (Adder1)
    - and to compute address (Adder2)
  - Memory used for instruction and data

# Reality Check: Intel 8086 clock cycles

## Arithmetic

3	add	reg16, reg16	
118-133	mul	dx:ax, reg16	<b>very slow!!</b>
128-154	imul	dx:ax, reg16	
114-162	div	dx:ax, reg16	
165-184	idiv	dx:ax, reg16	

## Data Transfer

14	mov	reg16, mem16
15	mov	mem16, reg16

## Conditional Branch


4/16	je	displacement8
------	----	---------------

## Unconditional Jump

15	jmp	segment:offset16
----	-----	------------------




# Multi-cycle Datapath

 

**Multi-cycle = 1 ALU + Controller**

# Multi-cycle Datapath: with controller

 

# Multi-cycle: 5 execution steps



Source: Chipworks, Inc.

From: Siemens SAB80C535-N  
8-bit Microcontroller



- **T<sub>1</sub> (a,lw,sw,beq,j) Instruction Fetch**
- **T<sub>2</sub> (a,lw,sw,beq,j) Instruction Decode and Register Fetch**
- **T<sub>3</sub> (a,lw,sw,beq,j) Execution, Memory Address Calculation, or Branch Completion**
- **T<sub>4</sub> (a,lw,sw)      Memory Access or R-type instruction completion**
- **T<sub>5</sub> (a,lw)      Write-back step**

***INSTRUCTIONS TAKE FROM 3 - 5 CYCLES!***

# Multi-cycle Approach

All operations in each clock cycle  $T_i$  are done in parallel not sequential!


For example,  $T_1$ ,  $IR = \text{Memory}[PC]$  and  $PC = PC + 4$  are done simultaneously!

	Step name	Action for R-type instructions	Action for memory-reference instructions	Action for branches	Action for jumps
$T_1$	Instruction fetch		$IR = \text{Memory}[PC]$ $PC = PC + 4$		
$T_2$	Instruction decode/register fetch		$A = \text{Reg}[IR[25-21]]$ $B = \text{Reg}[IR[20-16]]$ $ALUOut = PC + (\text{sign-extend}(IR[15-0]) \ll 2)$		
$T_3$	Execution, address computation, branch/jump completion	$ALUOut = A \text{ op } B$	$ALUOut = A + \text{sign-extend}(IR[15-0])$	if ( $A == B$ ) then $PC = ALUOut$	$PC = PC[31-28] \parallel (IR[25-0]\ll2)$
$T_4$	Memory access or R-type completion	$\text{Reg}[IR[15-11]] = ALUOut$	Load: $MDR = \text{Memory}[ALUOut]$ or Store: $\text{Memory}[ALUOut] = B$		
$T_5$	Memory read completion		Load: $\text{Reg}[IR[20-16]] = MDR$		


Between Clock  $T_2$  and  $T_3$  the microcode sequencer will do a dispatch 1

# Multi-cycle using Microprogramming
 
## Finite State Machine ( *hardwired control* )



## Microcode controller

 

**Requires microcode memory  
to be faster than main memory**

# Microcode: Trade-offs



- Distinction between specification and implementation is sometimes blurred
- Specification Advantages:
  - Easy to design and write (maintenance)
  - Design architecture and microcode in parallel
- Implementation (off-chip ROM) Advantages
  - Easy to change since values are in memory
  - Can emulate other architectures
  - Can make use of internal registers
- Implementation Disadvantages, SLOWER now that:
  - Control is implemented on same chip as processor
  - ROM is no longer faster than RAM
  - No need to go back and make changes

# Microinstruction format

Field name	Value	Signals active	Comment
ALU control	Add	ALUOp = 00	Cause the ALU to add.
	Subt	ALUOp = 01	Cause the ALU to subtract; this implements the compare for branches.
	Func code	ALUOp = 10	Use the instruction's function code to determine ALU control.
SRC1	PC	ALUSrcA = 0	Use the PC as the first ALU input.
	A	ALUSrcA = 1	Register A is the first ALU input.
SRC2	B	ALUSrcB = 00	Register B is the second ALU input.
	4	ALUSrcB = 01	Use 4 as the second ALU input.
	Extend	ALUSrcB = 10	Use output of the sign extension unit as the second ALU input.
	Extshft	ALUSrcB = 11	Use the output of the shift-by-two unit as the second ALU input.
Register control	Read		Read two registers using the rs and rt fields of the IR as the register numbers and putting the data into registers A and B.
	Write ALU	RegWrite, RegDst = 1, MemtoReg = 0	Write a register using the rd field of the IR as the register number and the contents of the ALUOut as the data.
	Write MDR	RegWrite, RegDst = 0, MemtoReg = 1	Write a register using the rt field of the IR as the register number and the contents of the MDR as the data.
Memory	Read PC	MemRead, lorD = 0	Read memory using the PC as address; write result into IR (and the MDR).
	Read ALU	MemRead, lorD = 1	Read memory using the ALUOut as address; write result into MDR.
	Write ALU	MemWrite, lorD = 1	Write memory using the ALUOut as address, contents of B as the data.
PC write control	ALU	PCSource = 00 PCWrite	Write the output of the ALU into the PC.
	ALUOut-cond	PCSource = 01, PCWriteCond	If the Zero output of the ALU is active, write the PC with the contents of the register ALUOut.
	jump address	PCSource = 10, PCWrite	Write the PC with the jump address from the instruction.
Sequencing	Seq	AddrCtl = 11	Choose the next microinstruction sequentially.
	Fetch	AddrCtl = 00	Go to the first microinstruction to begin a new instruction.
	Dispatch 1	AddrCtl = 01	Dispatch using the ROM 1.
	Dispatch 2	AddrCtl = 10	Dispatch using the ROM 2.

# Microinstruction format: Maximally vs. Minimally Encoded




- **No encoding:**
  - 1 bit for each datapath operation
  - faster, requires more memory (logic)
  - used for Vax 780 — an astonishing 400K of memory!
- **Lots of encoding:**
  - send the microinstructions through logic to get control signals
  - uses less memory, slower
- **Historical context of CISC:**
  - Too much logic to put on a single chip with everything else
  - Use a ROM (or even RAM) to hold the microcode
  - It's easy to add new instructions

# Microprogramming: program

Label	ALU control	SRC1	SRC2	Register control	Memory	PCWrite control	Sequencing
Fetch	Add	PC	4		Read PC	ALU	Seq
	Add	PC	Extshft	Read			Dispatch 1
Mem1	Add	A	Extend				Dispatch 2
LW2					Read ALU		Seq
				Write MDR			Fetch
SW2					Write ALU		Fetch
Rformat1	Func code	A	B				Seq
				Write ALU			Fetch
BEQ1	Subt	A	B			ALUOut-cond	Fetch
JUMP1						Jump address	Fetch


Step name	Action for R-type instructions	Action for memory-reference instructions	Action for branches	Action for jumps
Instruction fetch		IR = Memory[PC] PC = PC + 4		
Instruction decode/register fetch		A = Reg [IR[25-21]] B = Reg [IR[20-16]] ALUOut = PC + (sign-extend (IR[15-0]) << 2)		
Execution, address computation, branch/jump completion	ALUOut = A op B	ALUOut = A + sign-extend (IR[15-0])	if (A == B) then PC = ALUOut	PC = PC [31-28]    (IR[25-0]<<2)
Memory access or R-type completion	Reg [IR[15-11]] = ALUOut	Load: MDR = Memory[ALUOut] or Store: Memory [ALUOut] = B		
Memory read completion		Load: Reg[IR[20-16]] = MDR		

# Microprogramming: program overview

 
 
# Microprogram stepping: T<sub>1</sub> Fetch


(Done in parallel) IR←MEMORY[PC] & PC ← PC + 4



Label	ALU	SRC1	SRC2	RCntl	Memory	PCwrite	Seq
Fetch add	pc	4			ReadPC	ALU	Seq
 
# $T_2$ Fetch + 1


$A \leftarrow \text{Reg}[\text{IR}[25-21]] \& B \leftarrow \text{Reg}[\text{IR}[20-16]] \& \text{ALUOut} \leftarrow \text{PC} + \text{signext}(\text{IR}[15-0]) \ll 2$



<u>Label</u>	<u>ALU</u>	<u>SRC1</u>	<u>SRC2</u>	<u>RCntl</u>	<u>Memory</u>	<u>PCwrite</u>	<u>Seq</u>
	add	pc	ExtSh	Read			D#1
 
# T<sub>3</sub> Dispatch 1: Mem1


$$\text{ALUOut} \leftarrow A + \text{sign\_extend}(\text{IR}[15-0])$$



<u>Label</u>	<u>ALU</u>	<u>SRC1</u>	<u>SRC2</u>	<u>RCntl</u>	<u>Memory</u>	<u>PCwrite</u>	<u>Seq</u>
Mem1 add	A		ExtSh				D#2

# T<sub>4</sub> Dispatch 2: LW2


MDR ← Memory[ALUOut]

 

<u>Label</u>	<u>ALU</u>	<u>SRC1</u>	<u>SRC2</u>	<u>RCntl</u>	<u>Memory</u>	<u>PCwrite</u>	<u>Seq</u>
LW2					ReadALU		Seq

# T<sub>5</sub> LW2+1

Reg[ IR[20-16] ] ← MDR

 


Label ALU SRC1 SRC2 RCntl Memory  
WMDR

PCwrite

Seq  
Fetch

# T<sub>4</sub> Dispatch 2: SW2


Memory[ ALUOut ] ← B

 

<u>Label</u>	<u>ALU</u>	<u>SRC1</u>	<u>SRC2</u>	<u>RCntl</u>	<u>Memory</u>	<u>PCwrite</u>	<u>Seq</u>
SW2					WriteALU		Fetch
 
# T<sub>3</sub> Dispatch 1: Rformat1


**ALUOut**  $\leftarrow$  A op(IR[31-26]) B



<u>Label</u>	<u>ALU</u>	<u>SRC1</u>	<u>SRC2</u>	<u>RCntl</u>	<u>Memory</u>	<u>PCwrite</u>	<u>Seq</u>
Rf...1	op	A	B				Seq

# T<sub>4</sub> Dispatch 1: Rformat1+1

Reg[ IR[15-11] ] ← ALUOut

 


Label ALU SRC1 SRC2 RCntl Memory  
WALU

PCwrite

Seq  
Fetch
 
# T<sub>3</sub> Dispatch 1: BEQ1


If ( $A - B == 0$ ) { PC  $\leftarrow$  ALUOut; }



Label	ALU	SRC1	SRC2	RCntl	Memory
BEQ1 subt	A	B			

PCwrite	Seq
ALUOut-0	Fetch

# T<sub>3</sub> Dispatch 1: Jump1

 

<u>Label</u>	<u>ALU</u>	<u>SRC1</u>	<u>SRC2</u>	<u>RCntl</u>	<u>Memory</u>
Jump1					

<u>PCwrite</u>	<u>Jaddr</u>	<u>Seq</u>	<u>Fetch</u>

# The Big Picture

