



**EECS 316 CAD**  
**Computer Aided Design**

**LECTURE 2:**

**Delay models, std\_ulogic and  
with-select-when**

*Instructor: Francis G. Wolff  
wolff@eecs.cwru.edu*

*Chris Papachristou  
Case Western Reserve University*

# Review: Full Adder: Truth Table

- A *Full-Adder* is a *Combinational circuit* that forms the arithmetic sum of three input bits.
- It consists of three inputs ( $z, x, y$ ) and two outputs (*Carry*, *Sum*) as shown.

$z$	$x$	$y$	$c$	$s$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Truth Table

$z \backslash xy$	00	01	11	10
0		1		1
1	1		1	

$$s = x \oplus y \oplus z$$

$z \backslash xy$	00	01	11	10
0			1	
1		1	1	1

$$c = xy + xz + yz = xy + z(x \oplus y)$$

Karnaugh maps

# Review: Full Adder: Architecture

## Entity Declaration

```
ENTITY full_adder IS
  PORT (x, y, z:      IN std_logic;
        Sum, Carry:  OUT std_logic
  ); END full_adder;
```

Optional Entity END **name**;

## Architecture Declaration

```
ARCHITECTURE full_adder_arch_1 OF full_adder IS
BEGIN
  Sum <= ( ( x XOR y ) XOR z );
  Carry <= (( x AND y ) OR (z AND (x AND y)));
END full_adder_arch_1;
```

Optional Architecture END **name**;

# Review: SIGNAL: Scheduled Event



- **SIGNAL**

Like variables in a programming language such as C, signals can be assigned values, e.g. 0, 1

- **However, SIGNALs also have an associated time value**

A signal receives a value at a specific point in time and retains that value until it receives a new value


at a future point in time (**i.e. scheduled event**)

- The **waveform of the signal** is


a sequence of values assigned to a signal over time

- **For example**

 wave <= '0', '1' after 10 ns, '0' after 15 ns, '1' after 25 ns;


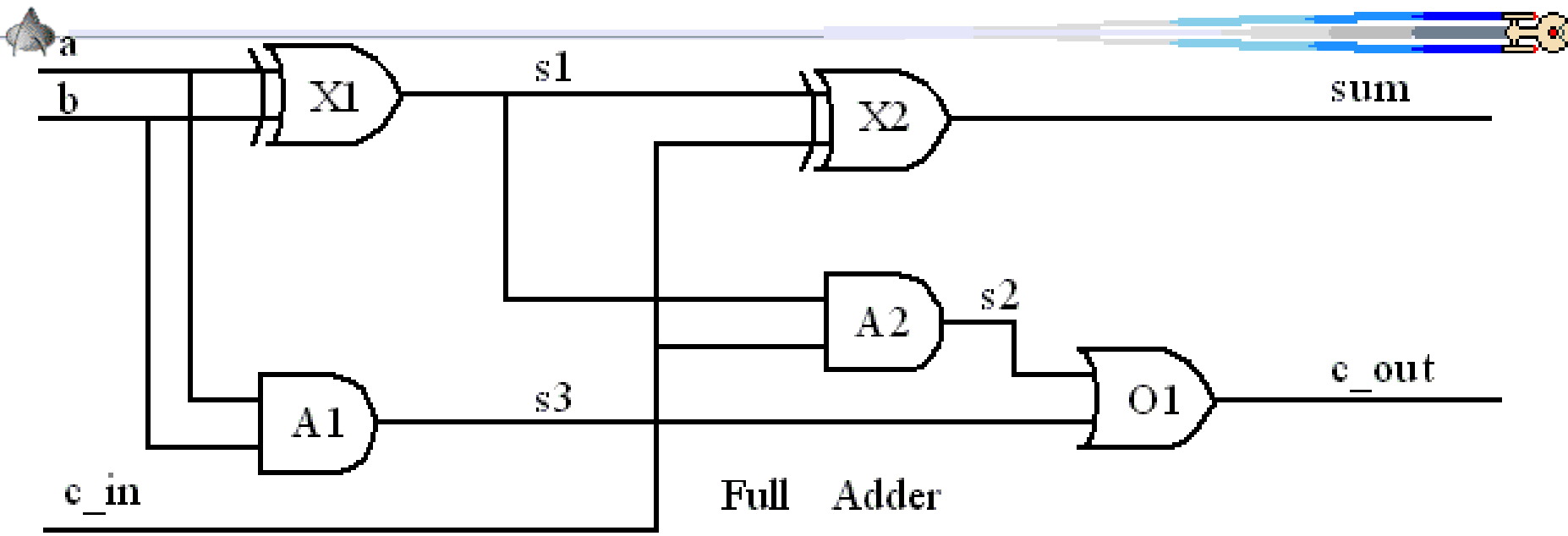
# Review: Full Adder: Architecture with Delay



```
ARCHITECTURE full_adder_arch_2 OF full_adder IS
    SIGNAL S1, S2, S3: std_logic;
BEGIN
    s1    <= ( a XOR b )      after 15 ns;
    s2    <= ( c_in AND s1 ) after 5 ns;
    s3    <= ( a AND b )     after 5 ns;
    Sum   <= ( s1 XOR c_in ) after 15 ns;
    Carry <= ( s2 OR s3 )    after 5 ns;
END;
```

Signals (like wires) are not PORTs they do not have direction (i.e. IN, OUT)

# Signal order: Does it matter? No

```
ARCHITECTURE full_adder_arch_2 OF full_adder IS
    SIGNAL S1, S2, S3: std_logic;
BEGIN
    s1    <= ( a XOR b )      after 15 ns;
    s2    <= ( c_in AND s1 ) after 5 ns;
    s3    <= ( a AND b )     after 5 ns;
    Sum   <= ( s1 XOR c_in ) after 15 ns;
    Carry <= ( s2 OR s3 )    after 5 ns;
END;
```

```
ARCHITECTURE full_adder_arch_3 OF full_adder IS
    SIGNAL S1, S2, S3: std_logic;
BEGIN
    Carry <= ( s2 OR s3 )    after 5 ns;
    Sum   <= ( s1 XOR c_in ) after 15 ns;
    s3    <= ( a AND b )     after 5 ns;
    s2    <= ( c_in AND s1 ) after 5 ns;
    s1    <= ( a XOR b )     after 15 ns;
END;
```

No,  
this  
is not  
C!

Net-  
lists  
have  
same  
behav-  
ior  
&  
parall-  
el

# Delta Delay


- **Default signal assignment propagation delay if no delay is explicitly prescribed**
  - **VHDL signal assignments do not take place immediately**
  - **Delta is an infinitesimal VHDL time unit so that all signal assignments can result in signals assuming their values at a future time**
  - **E.g.**

```
Output <= NOT Input ;  
-- Output assumes new value in one delta cycle
```
- **Supports a model of concurrent VHDL process execution**
  - **Order in which processes are executed by simulator does not affect simulation output**

# Delta Delay

## An Example with Delta Delay

- What is the behavior of C?

 

### Using delta delay scheduling

<u>Time</u>	<u>Delta</u>	<u>Event</u>
0 ns	1	IN: 1->0 eval INVERTER
	2	A: 0->1 eval NAND, AND
	3	B: 1->0 C: 0->1 eval AND
	4	C: 1->U
1 ns		



# Inertial Delay


- Provides for specification propagation delay and input pulse width, i.e. 'inertia' of output:

```
target <= [REJECT time_expression] INERTIAL waveform;
```


- Inertial delay is default and REJECT is optional :

```
Output <= NOT Input AFTER 10 ns;  

 -- Propagation delay and minimum pulse width are 10ns
```


 
# Inverter model: lowpass filter (inertial)




**Short pulses = High frequency  
which get filtered out by cmos  
capacitance**

**Long pulses = low frequency  
which pass through**

 
# Transport Delay

- Transport delay must be explicitly specified
  - I.e. keyword “TRANSPORT” must be used
- Signal will assume its new value after specified delay

```
-- TRANSPORT delay example
Output <= TRANSPORT NOT Input AFTER 10 ns;
```



# Inertial and Transport Delay

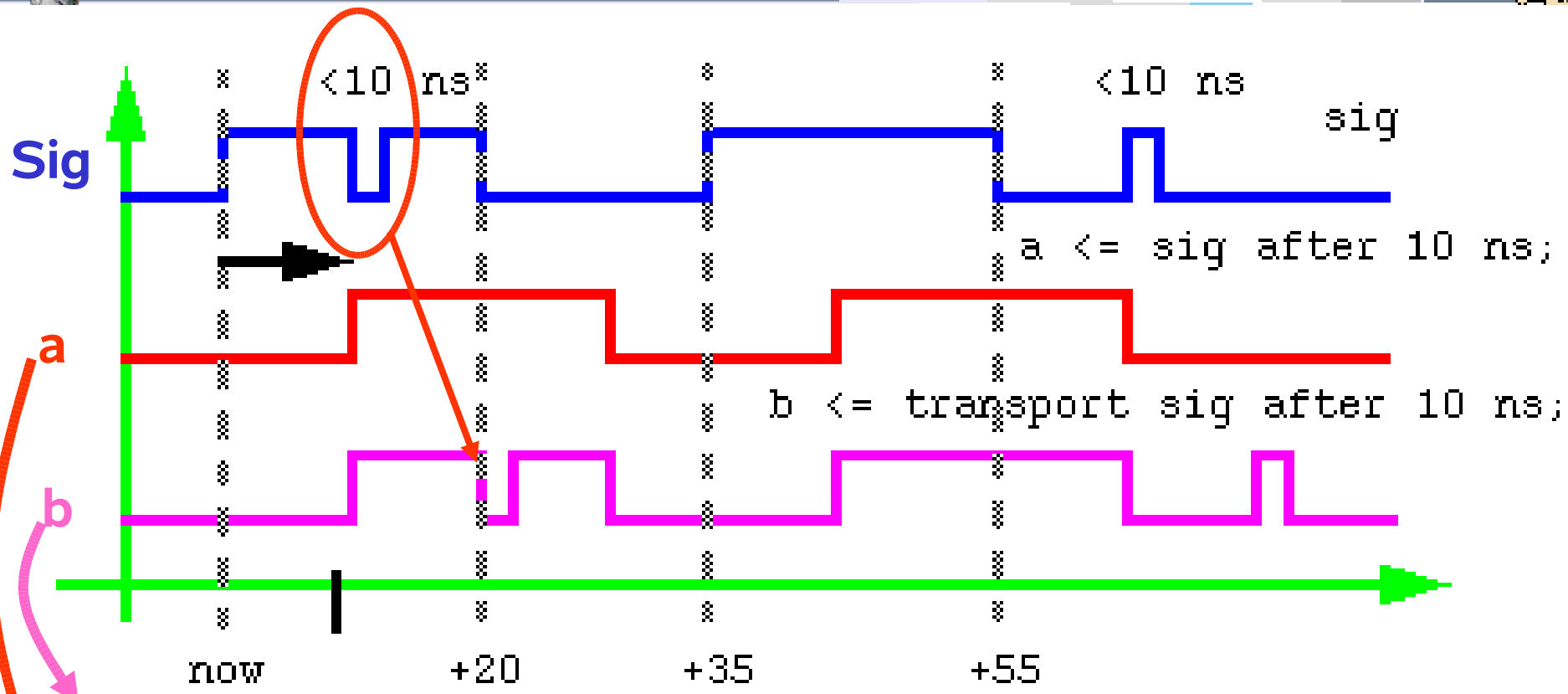

**Transport Delay** is useful for modeling data buses, networks

**Inertial Delay** is useful for modeling logic gates

# Combinatorial Logic Operators




## #Transistors

2	<b>NOT</b>	$z \leq \text{NOT } (x); \quad z \leq \text{NOT } x;$
$2+2i$	<b>AND</b>	$z \leq x \text{ AND } y;$
$2i$	<b>NAND</b>	$z \leq \text{NOT } (x \text{ AND } y);$
$2+2i$	<b>OR</b>	$z \leq x \text{ OR } y;$
$2i$	<b>NOR</b>	$z \leq \text{NOT } (x \text{ OR } y);$
10	<b>XOR</b>	$z \leq (x \text{ and NOT } y) \text{ OR } (\text{NOT } x \text{ AND } y);$ $z \leq (x \text{ AND } y) \text{ NOR } (x \text{ NOR } y); \text{ --AOI}$
12	<b>XNOR</b>	$z \leq (x \text{ and } y) \text{ OR } (\text{NOT } x \text{ AND NOT } y);$ $z \leq (x \text{ NAND } y) \text{ NAND } (x \text{ OR } y); \text{ --OAI}$

Footnote: ( $i$ =#inputs) We are only referring to CMOS static transistor ASIC gate designs  
Exotic XOR designs can be done in 6 (J. W. Wang, IEEE J. Solid State Circuits, 29, July 1994)

# Std\_logic AND: Un-initialized value

 

NOT	0	1	U
	1	0	U

AND	0	1	U
0	0	0	0
1	0	1	U
U	0	U	U

OR	0	1	U
0	0	1	U
1	1	1	1
U	U	1	U


0 AND <anything> is 0

0 NAND <anything> is 1

1 OR <anything> is 1

1 NOR <anything> is 0

# SR Flip-Flop (Latch)

 


NOR

R	S	$Q_{n+1}$
0	0	$Q_n$
0	1	1
1	0	0
1	1	U

$$Q \leftarrow R \text{ NOR } \overline{Q};$$
 
$$\overline{Q} \leftarrow S \text{ NOR } Q;$$



NAND

R	S	$Q_{n+1}$
0	0	U
0	1	1
1	0	0
1	1	$Q_n$



$$Q \leftarrow R \text{ NAND } \overline{Q};$$

$$\overline{Q} \leftarrow S \text{ NAND } Q;$$

# SR Flip-Flop (Latch)



NAND		
R	S	$Q_{n+1}$
0	0	U
0	1	1
1	0	0
1	1	$Q_n$

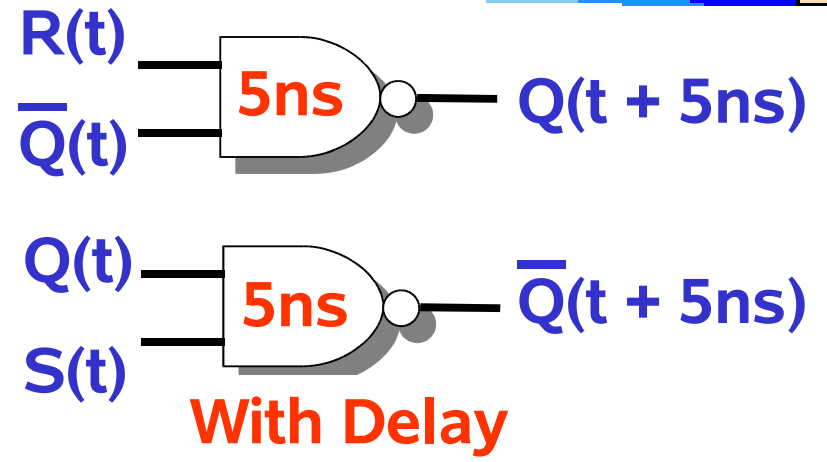 


Example: R <= '1', '0' after 10ns, '1' after 30ns; S <= '1';

t	0	5ns	10ns	15ns	20ns	25ns	30ns	35ns	40ns
R	1	1	0	0	0	0	1	1	1
Q-bar	U	U	U	U	0	0	0	0	0
Q	U	U	U	1	1	1	1	1	1
S	1	1	1	1	1	1	1	1	1


 
# Std\_logic AND: X Forcing Unknown Value



NOT	0	X	1	U
	1	X	0	U

AND	0	X	1	U
0	0	0	0	0
X	0	X	X	U
1	0	X	1	U
U	0	U	U	U

OR	0	X	1	U
0	0	X	1	U
X	X	X	1	U
1	1	1	1	1
U	U	U	1	U

0 AND <anything> is 0

0 NAND <anything> is 1


1 OR <anything> is 1

0 NOR <anything> is 1

# The rising transition signal



$V_{CC}=5.5$   $25^{\circ}\text{C}$

 

Unknown  
2.20 Volt  
gap

# Modeling logic gate values: std\_ulogic



TYPE **std\_ulogic** IS ( -- Unresolved LOGIC

‘Z’, -- High Impedance (Tri-State)

‘1’, -- Forcing 1

‘H’, -- Weak 1

‘X’, -- Forcing Unknown: i.e. combining 0 and 1

‘W’, -- Weak Unknown: i.e. combining H and L


‘L’, -- Weak 0

‘0’, -- Forcing 0

‘U’, -- Un-initialized

‘-’, -- Don't care

);

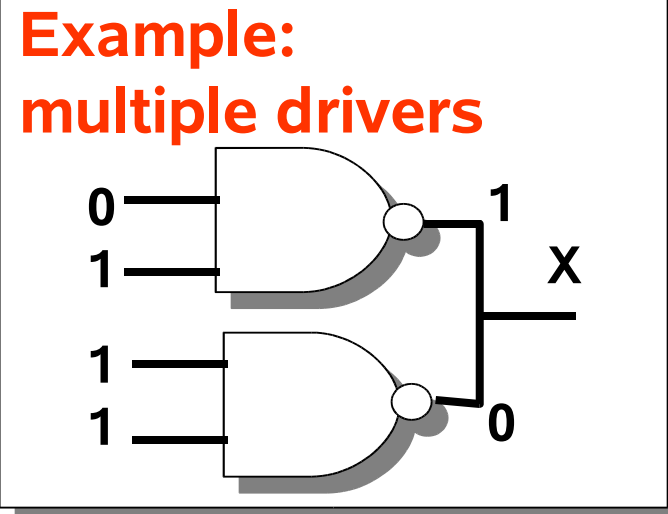

# Multiple output drivers: Resolution Function

	U	X	0	L	Z	W	H	1	-
U	U	U	U	U	U	U	U	U	U
X	U	X	X	X	X	X	X	X	X
0	U	X	0	0	0	0	0	X	X
L									
Z									
W									
H									
1									
-	U	X	X	X	X	X	X	X	X

Suppose that  
 the first gate outputs a **1**  
 the second gate outputs a **0**  
 then  
 the mult-driver output is **X**  
**X: forcing unknown value by combining 1 and 0 together**

# Multiple output drivers: Resolution Function




	U	X	0	L	Z	W	H	1	-
U	U	U	U	U	U	U	U	U	U
X		X	X	X	X	X	X	X	X
0			0	0	0	0	0	X	X
L				L	L	W	W	1	X
Z					Z	W	H	1	X
W						W	W	1	X
H							H	1	X
1								1	X
-									X

Observe that 0 pulls down all weak signals to 0

H <driving> L => W

- Note the multi-driver resolution table is symmetrical
 
# Resolution Function: std\_logic buffer gate




input:	U	0	L	W	X	Z	H	1	-
output:	U	0	0	X	X	X	1	1	X

**0 or L becomes 0**

**Transition zone becomes X**

**H or 1 becomes 1**

# Resolving input: std\_logic AND GATE

 

Process each input as an unresolved to resolved buffer.

Then process the gate as a standard logic gate { 0, X, 1, U }


For example, let's transform `z <= 'W' AND '1';`

`z <= 'W' AND '1';` -- convert `std_ulogic 'W'` to `std_logic 'X'`

`z <= 'X' AND '1';` -- now compute the `std_logic AND`

`z <= 'X';`

# 2-to-1 Multiplexor: with-select-when

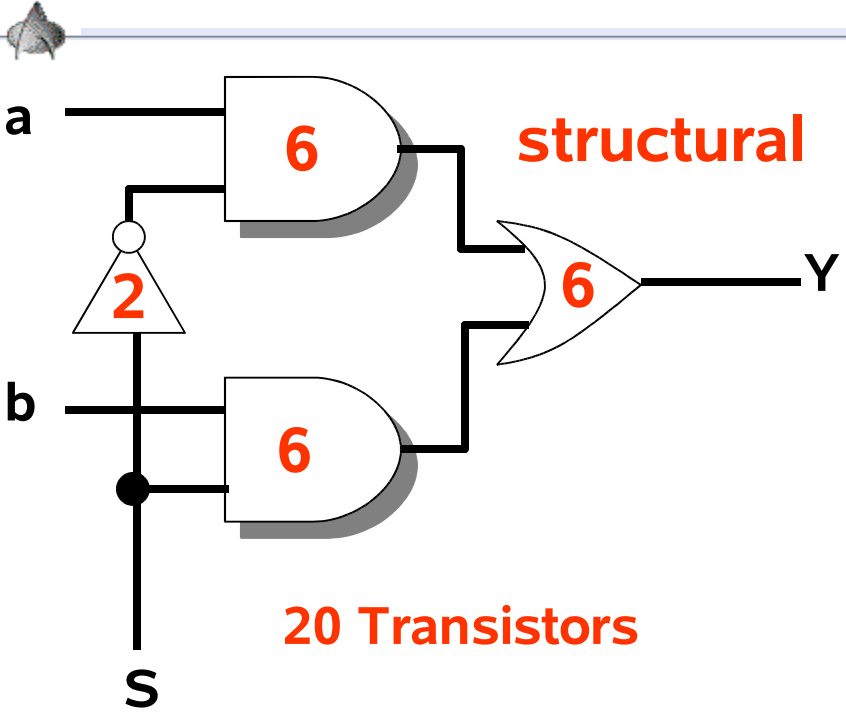


structural

20 Transistors

combinatorial logic
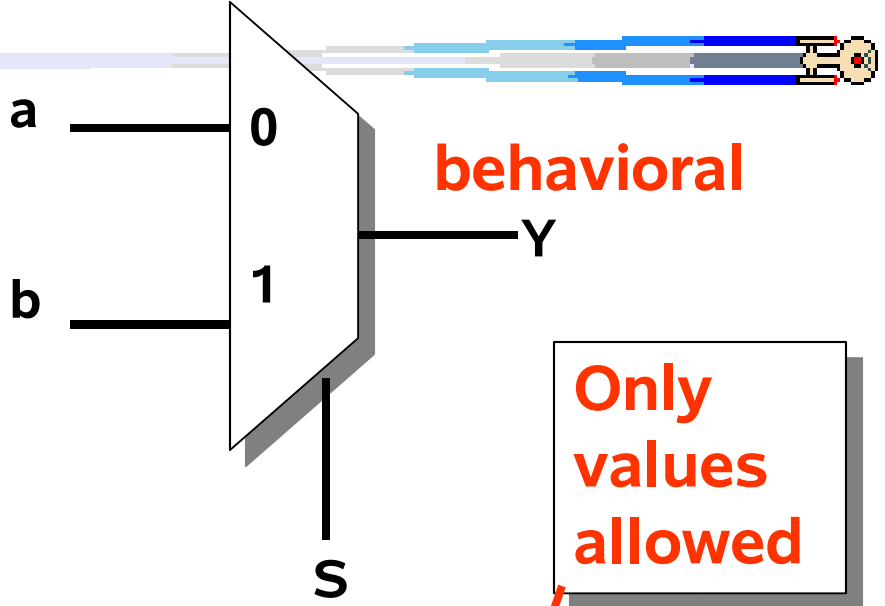
```
Y <= (a AND NOT s)
      OR
      (b AND s);
```



behavioral

Only values allowed

```
WITH s SELECT
  Y <= a WHEN '0',
      b WHEN '1';
```

or more general

```
WITH s SELECT
  Y <= a WHEN '0',
      b WHEN OTHERS;
```

OTHERS includes 1,U,L,W,X,H,Z




# 4-to-1 Multiplexor: with-select-when
 
## Structural Combinatorial logic

```
Y <= sa OR sb OR sc OR sd;  
sa <= a AND ( NOT s(1) AND NOT s(0) );  
sb <= b AND ( NOT s(1) AND s(0) );  
sc <= c AND ( s(1) AND NOT s(0) );  
sd <= d AND ( s(1) AND s(0) );
```

As the complexity of the combinatorial logic **grows**, the SELECT statement, **simplifies** logic design but at a **loss** of structural information




```
WITH s SELECT  
Y <= a WHEN "00",  
b WHEN "01",  
c WHEN "10",  
d WHEN OTHERS;
```

Note the comma after WHEN


behavioral

# with-select-when: 2 to 4-line Decoder

 

Replace this  
with a NOR,  
then 26 total  
transistors

 
```
SIGNAL S: std_logic_vector(1 downto 0);  
SIGNAL Y: std_logic_vector(3 downto 0);
```



WITH **S** SELECT

```
Y <= "1000" WHEN "11",  
     "0100" WHEN "10",  
     "0010" WHEN "01",  
     "0001" WHEN OTHERS;
```

# Tri-State buffer

 

```
ENTITY TriStateBuffer IS
    PORT(x:      IN      std_logic;
          y:      OUT     std_logic;
          oe:     IN      std_logic
    ); END;
```

```
ARCHITECTURE Buffer3 OF TriStateBuffer IS
BEGIN
```


```
    WITH oe SELECT
```

```
    y <= x WHEN '1', -- Enabled: y <= x;
```

```
    'Z' WHEN OTHERS; -- Disabled: output a tri-state
```

```
END;
```

# Inverted Tri-State buffer

 

```
ENTITY TriStateBufferNot IS
    PORT(x:      IN      std_logic;
          y:      OUT     std_logic;
          oe:     IN      std_logic
    ); END;
```


```
ARCHITECTURE Buffer3 OF TriStateBufferNot IS
BEGIN
```

```
    WITH oe SELECT
```

```
    y <= NOT(x) WHEN '1', -- Enabled: y <= Not(x);
        'Z'      WHEN OTHERS; -- Disabled
```

```
END;
```

# ROM: 4 byte Read Only Memory

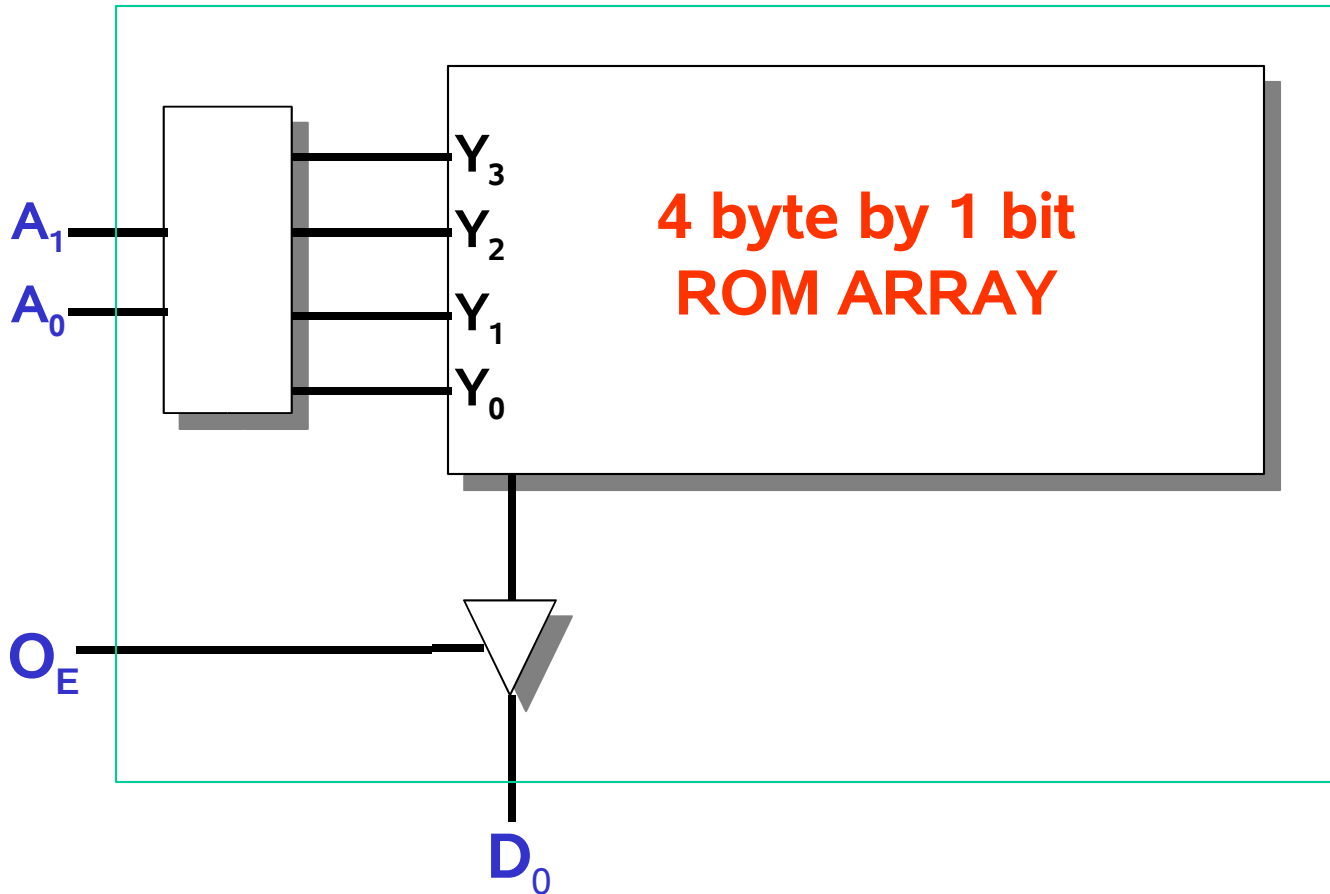

# ROM: 4 byte Read Only Memory

```
ENTITY rom_4x1 IS
```

```
    PORT(A:      IN std_logic_vector(1 downto 0);
```

```
         OE:     IN std_logic; -- Tri-State Output
```

```
         D:      OUT std_logic
```

```
); END;
```

```
ARCHITECTURE rom_4x1_arch OF rom_4x1 IS
```

```
    SIGNAL ROMout: std_logic;
```

```
BEGIN
```

```
    BufferOut: TriStateBuffer PORT MAP(ROMout, D, OE);
```

```
    WITH A SELECT
```

```
        ROMout <= '1' WHEN "00",
```

```
                '0' WHEN "01",
```


```
                '0' WHEN "10",
```

```
                '1' WHEN "11";
```

Component Instance



Component  
declaration  
name



# Component Declaration/Instance relationship

ARCHITECTURE rom\_4x1\_arch OF rom\_4x1 IS

**COMPONENT** TriStateBuffer

PORT (x: IN std\_logic; y: OUT std\_logic, oe: IN std\_logic);  
END COMPONENT;

Component Declaration

SIGNAL ROMout: std\_logic;

BEGIN

BufferOut: TriStateBuffer PORT MAP(ROMout, D, OE);

Colon (:) says make a  
Component Instance


WITH A SELECT

ROMout <= '1' WHEN "00",  
'0' WHEN "01",  
'0' WHEN "10",  
'1' WHEN "11";

Component Instance  
Name: *BufferOut*

END;

# Component Port relationship

 

OE → IN → oe → IN

D → OUT → y → OUT

```

COMPONENT TriStateBuffer
  PORT (x: IN std_logic; y: OUT std_logic, oe: IN std_logic);
END COMPONENT;
  
```

```


BufferOut: TriStateBuffer    PORT MAP(ROMout, D, OE);
  
```

```

ENTITY rom_4x1 IS
  PORT(A:    IN std_logic_vector(1 downto 0);
        OE:  IN std_logic; -- Tri-State Output
        D:   OUT std_logic
  ); END;
  
```



# Assignment #2 (Part 1 of 3)

 

1) Assume each gate is 5 ns delay for the above circuit.

(a) Write entity-architecture for a inertial model

(b) Given the following waveform, draw, R, S, Q, NQ (**inertial**)

R  $\leftarrow$  '1', '0' after 25 ns, '1' after 30 ns, '1' after 50 ns;


S  $\leftarrow$  '0', '1' after 20 ns, '0' after 35 ns, '1' after 50 ns;

(c) Repeat (b) but now assume each gate is 20 ns delay

(d) Write entity-architecture for a transport model

(e) Given the waveform in (b) draw, R, S, Q, NQ (**transport**)

# Assignment #2 (Part 2 of 3)

 

(2) Given the above two tri-state buffers connected together (assume transport model of 5ns per gate), draw **X**, **Y**, **F**, **a**, **b**, **G** for the following input waveforms:

**X** <= '1', '0' after 10 ns, 'X' after 20 ns, 'L' after 30 ns, '1' after 40 ns;

**Y** <= '0', 'L' after 10 ns, 'W' after 20 ns, '0' after 30 ns, 'Z' after 40 ns;

**F** <= '0', '1' after 10 ns, '0' after 50 ns;

# Assignment #2 (Part 3 of 3)



3) Write (**no programming**) a entity-architecture for a **1-bit** ALU. The input will consist of **x**, **y**, **C<sub>in</sub>**, **f** and the output will be **S** and **C<sub>out</sub>**. Make **components** for 1-bit add/sub. The input function **f** (with-select) will enable the following operations:

<u>function f</u>	<u>ALU bit operation</u>
000	$S = 0; C_{out} = 0$
001	$S = x$
010	$S = y; C_{out} = 1;$
011	$S = C_{in}; C_{out} = x$
100	$S = x \text{ OR } y; C_{out} = x;$
101	$S = x \text{ AND } y; C_{out} = x;$
110	$(C_{out}, S) = x + y + C_{in};$ <b>(component)</b>
111	$(C_{out}, S) = \text{full subtractor}$ <b>(component)</b>

