



**EECS 318 CAD**  
**Computer Aided Design**

**LECTURE 3:**  
**The VHDL N-bit Adder**

*Instructor: Francis G. Wolff*  
*wolff@eecs.cwru.edu*

*Case Western Reserve University*

# Full Adder: Truth Table

- A *Full-Adder* is a *Combinational circuit* that forms the arithmetic sum of three input bits.
- It consists of three inputs ( $z, x, y$ ) and two outputs (*Carry*, *Sum*) as shown.

$z$	$x$	$y$	$c$	$s$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Truth Table

$z \backslash xy$	00	01	11	10
0		1		1
1	1		1	

$$s = x \oplus y \oplus z$$

$z \backslash xy$	00	01	11	10
0			1	
1		1	1	1

$$c = xy + xz + yz = xy + z(x \oplus y)$$

Karnaugh maps

# Combinatorial Logic Operators



**NOT**             $z \leftarrow \text{NOT } (x); \quad z \leftarrow \text{NOT } x;$

**AND**             $z \leftarrow x \text{ AND } y;$

**NAND**            $z \leftarrow \text{NOT } (x \text{ AND } y);$

**OR**               $z \leftarrow x \text{ OR } y;$

**NOR**             $z \leftarrow \text{NOT } (x \text{ OR } Y);$

**XOR**             $z \leftarrow (x \text{ and NOT } y) \text{ OR } (\text{NOT } x \text{ AND } y);$

**XNOR**            $z \leftarrow (x \text{ and } y) \text{ OR } (\text{NOT } x \text{ AND NOT } y);$

# Full Adder: Architecture

Entity Declaration

```
ENTITY full_adder IS  
  PORT (x, y, z:      IN std_logic;  
        Sum, Carry:  OUT std_logic  
); END full_adder;
```

Optional Entity END **name**;

Architecture Declaration

```
ARCHITECTURE full_adder_arch_1 OF full_adder IS  
BEGIN  
  Sum <= ( ( x XOR y ) XOR z );  
  Carry <= (( x AND y ) OR (z AND (x AND y)));  
END full_adder_arch_1;
```

Optional Architecture END **name**;

# SIGNAL: Scheduled Event

- **SIGNAL**

Like variables in a programming language such as C, signals can be assigned values, e.g. 0, 1

- **However, SIGNALs also have an associated time value**


A signal receives a value at a specific point in time and retains that value until it receives a new value at a future point in time (**i.e. scheduled event**)

- **The waveform of the signal is**


a sequence of values assigned to a signal over time

- **For example**

 wave  $\leq$  '0', '1' after 10 ns, '0' after 15 ns, '1' after 25 ns;



# Full Adder: Architecture with Delay

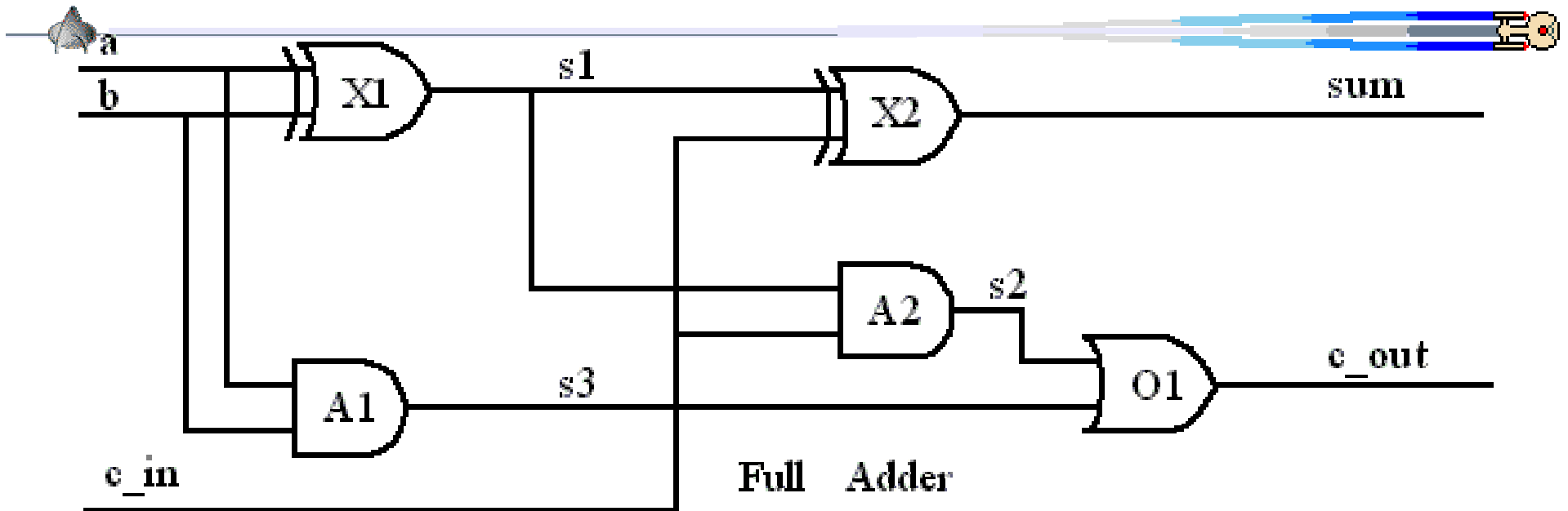

ARCHITECTURE **full\_adder\_arch\_2** OF **full\_adder** IS

SIGNAL **S1, S2, S3**: std\_logic;

BEGIN

**s1** <= ( **a XOR b** ) after 15 ns;

**s2** <= ( **c\_in AND s1** ) after 5 ns;

**s3** <= ( **a AND b** ) after 5 ns;

**Sum** <= ( **s1 XOR c\_in** ) after 15 ns;

**Carry** <= ( **s2 OR s3** ) after 5 ns;

END;

Signals (like wires) are not PORTs they do not have direction (i.e. IN, OUT)

# Signal order: Does it matter? No


```
ARCHITECTURE full_adder_arch_2 OF full_adder IS
    SIGNAL S1, S2, S3: std_logic;
BEGIN
    s1    <= ( a XOR b )      after 15 ns;
    s2    <= ( c_in AND s1 ) after 5 ns;
    s3    <= ( a AND b )     after 5 ns;
    Sum   <= ( s1 XOR c_in ) after 15 ns;
    Carry <= ( s2 OR s3 )    after 5 ns;
END;
```

```
ARCHITECTURE full_adder_arch_3 OF full_adder IS
    SIGNAL S1, S2, S3: std_logic;
BEGIN
    Carry <= ( s2 OR s3 )    after 5 ns;
    Sum   <= ( s1 XOR c_in ) after 15 ns;
    s3    <= ( a AND b )     after 5 ns;
    s2    <= ( c_in AND s1 ) after 5 ns;
    s1    <= ( a XOR b )     after 15 ns;
END;
```

No,  
this  
is  
not  
C!

Net-  
lists  
have  
same  
behav-  
ior  
&  
paral-  
lel
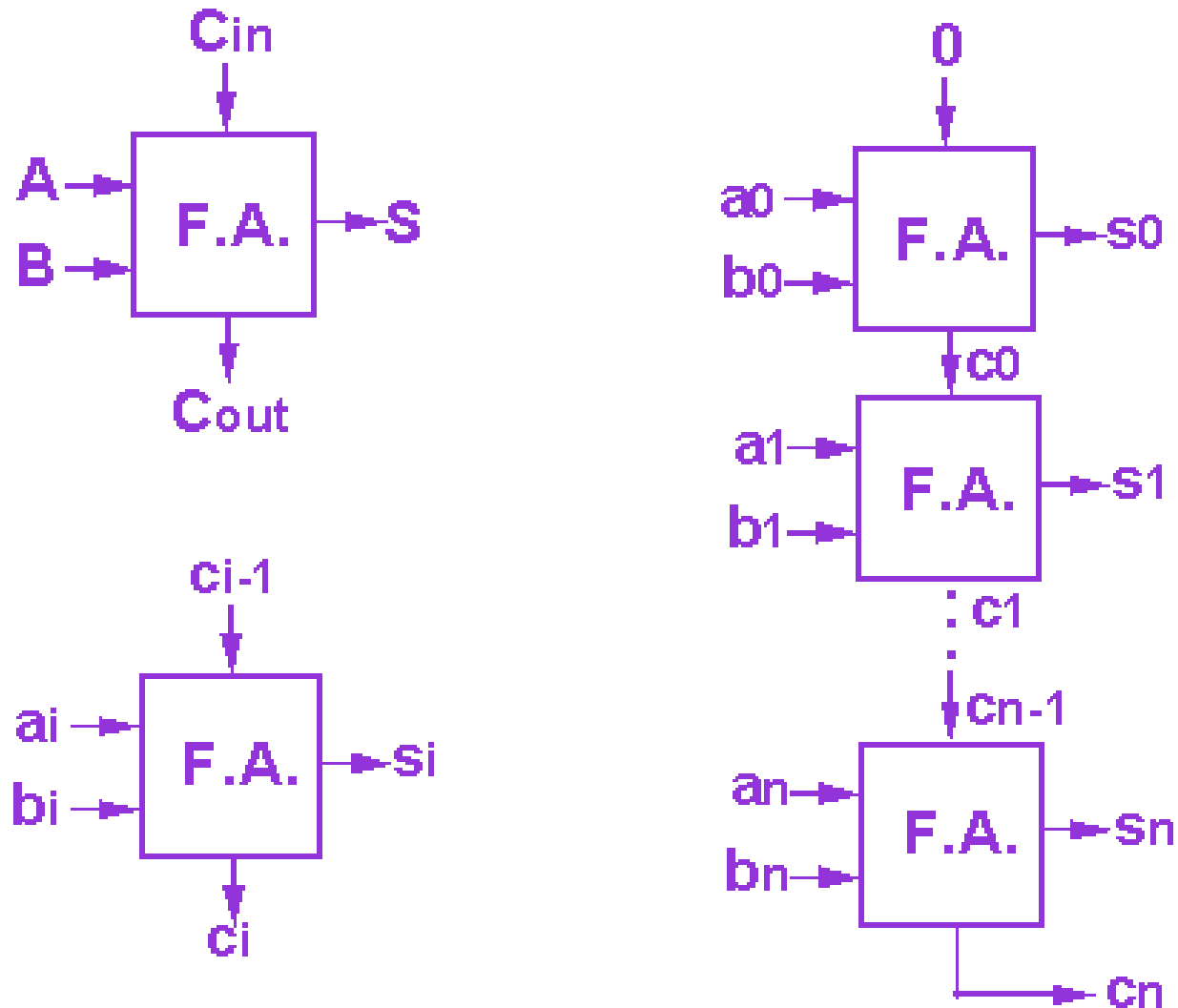
# The Ripple-Carry n-Bit Binary Parallel Adder





# Hierarchical design: 2-bit adder



- The design interface to a two bit adder is

```
LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;

ENTITY adder_bits_2 IS
    PORT (Cin:          IN    std_logic;
          a0, b0, a1, b1: IN    std_logic;
          S0, S1:      OUT   std_logic;
          Cout:        OUT   std_logic
    ); END;
```

- Note: that the ports are **positional dependant**  
(Cin, a0, b0, a1, b1, S0, S1, Cout)

# Hierarchical design: Component Instance



Component Declaration

```
ARCHITECTURE ripple_2_arch OF adder_bits_2 IS
  COMPONENT full_adder
    PORT (x, y, z: IN std_logic; Sum, Carry: OUT std_logic);
  END COMPONENT;
  SIGNAL t1: std_logic;
BEGIN
  FA1: full_adder PORT MAP (Cin, a0, b0, S0, t1);
  FA2: full_adder PORT MAP (t1, a1, b1, s1, Cout);
END;
```

Component instance #1 called FA1

Component instance #2 called FA2

# Positional versus Named Association



- **Positional Association** (must match the port order)

```
FA1: full_adder PORT MAP (Cin, a0, b0, S0, t1);
```

- **Named Association: signal => port\_name**

```
FA1: full_adder PORT
```

```
    MAP (Cin=>x, a0=>y, b0=>z, S0=>Sum, t1=>Carry);
```

```
FA1: full_adder PORT
```

```
    MAP (Cin=>x, a0=>y, b0=>z, t1=>Carry, S0=>Sum);
```

```
FA1: full_adder PORT
```

```
    MAP (t1=>Carry, S0=>Sum, a0=>y, b0=>z, Cin=>x);
```

# Component by Named Association



```
ARCHITECTURE ripple_2_arch OF adder_bits_2 IS
  COMPONENT full_adder
    PORT (x, y, z: IN std_logic; Sum, Carry: OUT std_logic);
  END COMPONENT;
  SIGNAL t1: std_logic; -- Temporary carry signal
BEGIN
  -- Named association
  FA1: full_adder PORT
    MAP (Cin=>x, a0=>y, b0=>z, S0=>Sum, t1=>Carry);

  -- Positional association
  FA2: full_adder PORT MAP (t1, a1, b1, s1, Cout);
END;
```

**-- Comments start with a double dash**

# Using vectors: std\_logic\_vector

```
ENTITY adder_bits_2 IS
  PORT (Cin:          IN  std_logic;
        a0, b0, a1, b1: IN  std_logic;
        S0, S1:      OUT std_logic;
        Cout:        OUT std_logic
  ); END;
```

- By using **vectors**, there is less typing of variables, a0, a1, ...

```
ENTITY adder_bits_2 IS
  PORT (Cin:          IN  std_logic;
        a, b:         IN  std_logic_vector(1 downto 0);
        S:            OUT std_logic_vector(1 downto 0);
        Cout:        OUT std_logic
  ); END;
```

# 2-bit Ripple adder using std\_logic\_vector



- Note, the signal variable usage is now different:  
**a0 becomes a(0)**

```
ARCHITECTURE ripple_2_arch OF adder_bits_2 IS
  COMPONENT full_adder
    PORT (x, y, z: IN std_logic; Sum, Carry: OUT std_logic);
  END COMPONENT;
  SIGNAL t1: std_logic; -- Temporary carry signal
BEGIN
  FA1: full_adder PORT MAP (Cin, a(0), b(0), S(0), t1);

  FA2: full_adder PORT MAP (t1, a(1), b(1), s(1), Cout);
END;
```

# 4-bit Ripple adder using std\_logic\_vector



ARCHITECTURE ripple\_4\_arch OF adder\_bits\_4 IS

COMPONENT full\_adder

PORT (x, y, z: IN std\_logic; Sum, Carry: OUT std\_logic);

END COMPONENT;

SIGNAL t: std\_logic\_vector(3 downto 1);

BEGIN

FA1: full\_adder PORT MAP (Cin, a(0), b(0), S(0), t(1));

FA2: full\_adder PORT MAP (t(1), a(1), b(1), S(1), t(2));

FA3: full\_adder PORT MAP (t(2), a(2), b(2), S(2), t(3));

FA4: full\_adder PORT MAP (t(3), a(3), b(3), S(3), Cout);

END;

- **std\_vectors** make it easier to replicate structures

# For-Generate statement: first improvement



ARCHITECTURE ripple\_4\_arch OF adder\_bits\_4 IS

COMPONENT full\_adder

PORT (x, y, z: IN std\_logic; Sum, Carry: OUT std\_logic);

END COMPONENT;

SIGNAL t: std\_logic\_vector(3 downto 1);

CONSTANT n: INTEGER := 4;

BEGIN

Constants never change value

FA1: full\_adder PORT MAP (Cin, a(0), b(0), S(0), t(1));

FA\_f: for i in 1 to n-2 generate

FA\_i: full\_adder PORT MAP (t(i), a(i), b(i), S(i), t(i+1));

end generate;

FA4: full\_adder PORT MAP (t(n), a(n), b(n), S(n), Cout);

END;

LABEL: before the for is not optional



# For-Generate statement: **second improvement**



ARCHITECTURE **ripple\_4\_arch** OF **adder\_bits\_4** IS

COMPONENT **full\_adder**

PORT (**x, y, z**: IN std\_logic; **Sum, Carry**: OUT std\_logic);

END COMPONENT;

SIGNAL **t**: std\_logic\_vector(4 downto 0);

CONSTANT **n**: INTEGER := 4;

BEGIN

**t(0) <= Cin;**      **Cout <= t(n);**

FA\_f: for **i** in 0 to **n-1** generate

**FA\_i: full\_adder** PORT MAP (**t(i), a(i), b(i), S(i), t(i+1)**);

end generate;

END;

Keep track of vector sizes

# N-bit adder using **generic**

```
ENTITY adder_bits_4 IS
  PORT (Cin:      IN   std_logic;
        a, b:    IN   std_logic_vector(3 downto 0);
        S:       OUT  std_logic_vector(3 downto 0);
        Cout:    OUT  std_logic
  ); END;
```

- By using **generics**, the design can be generalized

```
ENTITY adder_bits_n IS
  GENERIC(n:      INTEGER := 2);
  PORT (Cin:      IN   std_logic;
        a, b:    IN   std_logic_vector(n-1 downto 0);
        S:       OUT  std_logic_vector(n-1 downto 0);
        Cout:    OUT  std_logic
  ); END;
```

Default case is 2

# For-Generate statement: **third improvement**



```
ARCHITECTURE ripple_n_arch OF adder_bits_n IS
  COMPONENT full_adder
    PORT (x, y, z: IN std_logic; Sum, Carry: OUT std_logic);
  END COMPONENT;
  SIGNAL      t:  std_logic_vector(n downto 0);
BEGIN
  t(0)  <= Cin;      Cout <= t(n);
  FA: for i in 0 to n-1 generate
    FA_i: full_adder PORT MAP (t(i), a(i), b(i), S(i), t(i+1));
  end generate;
END;
```

# Stimulus Only Test Bench Architecture

## ARCHITECTURE tb OF tb\_adder\_4 IS

```
COMPONENT adder_bits_n
```

```
  GENERIC(n: INTEGER := 2);
```

```
  PORT (Cin: IN std_logic;
```

```
        a, b: IN std_logic_vector(n-1 downto 0);
```

```
        S: OUT std_logic_vector(n-1 downto 0);
```

```
        Cout: OUT std_logic
```

```
END COMPONENT;
```

```
SIGNAL x, y, Sum: std_logic_vector(n downto 0);
```

```
SIGNAL c, Cout: std_logic;
```

```
BEGIN
```

```
  x <= "0000", "0001" after 50 ns, "0101", after 100 ns;
```

```
  y <= "0010", "0011" after 50 ns, "1010", after 100 ns;
```

```
  c <= '1', '0' after 50 ns;
```

```
  UUT_ADDER_4: adder_bits_n GENERIC MAP(4)
```

```
    PORT MAP (c, x, y, Sum, Cout);
```

```
END;
```

Override  
default

# Stimulus Only Test Bench Entity



```
ENTITY tb_adder_4 IS
```

```
    PORT (Sum:      std_logic_vector(3 downto 0);
```

```
          Cout:    std_logic
```

```
); END;
```

The output of the testbench will be observe by the digital waveform of the simulator.