



EECS 318 CAD
Computer Aided Design



LECTURE 8:
VHDL PROCESSES

*Instructor: Francis G. Wolff
wolff@eecs.cwrn.edu*

Case Western Reserve University

This presentation uses powerpoint animation: please viewshow

  2-to-1 Multiplexor: and Datapath multiplexor




Datapath is n bits wide

WITH s SELECT
 $Y \leq a$ WHEN '0',
 b WHEN OTHERS;

WITH s SELECT
 $Y \leq a$ WHEN '0',
 b WHEN OTHERS;

Where is the difference?

 Generic 2-to-1 Datapath Multiplexor Entity



```
LIBRARY IEEE;  
USE IEEE.std_logic_1164.all;  
USE IEEE.std_logic_arith.all;
```

```
ENTITY Generic_Mux IS  
    GENERIC (n: INTEGER);  
    PORT (Y: OUT std_logic_vector(n-1 downto 0);  
          a: IN  std_logic_vector(n-1 downto 0);  
          b: IN  std_logic_vector(n-1 downto 0);  
          S: IN  std_logic_vector(0 downto 0)  
    );  
END ENTITY;
```

Generic 2-to-1 Datapath Multiplexor Architecture



```
ARCHITECTURE Generic_Mux_arch OF Generic_Mux IS  
BEGIN
```

```
    WITH S SELECT
```

```
        Y <= a WHEN "1",  
            b WHEN OTHERS;
```

```
END ARCHITECTURE;
```

```
CONFIGURATION Generic_Mux_cfg OF Generic_Mux IS
```


```
    FOR Generic_Mux_arch
```

```
        END FOR;
```

```
END CONFIGURATION;
```

Configurations are
require for simulation

Structural SR Flip-Flop (Latch)

 

NAND		
R	S	Q_{n+1}
0	0	U
0	1	1
1	0	0
1	1	Q_n

ENTITY **Latch** IS

 PORT(R, S: IN std_logic; Q, NQ: OUT std_logic);
END ENTITY;

ARCHITECTURE **latch_arch** OF **Latch** IS


BEGIN

Q <= **R** NAND **NQ**;

NQ <= **S** NAND **Q**;

END ARCHITECTURE;

 Inferring Behavioral Latches: Asynchronous



NAND		
R	S	Q_{n+1}
0	0	U
0	1	1
1	0	0
1	1	Q_n


Sensitivity list of signals:
Every time a change of state or event occurs on these signals this process will be called

ARCHITECTURE `Latch2_arch` OF `Latch` IS
BEGIN

```
PROCESS (R, S) BEGIN
  IF R = '0' THEN
    Q <= '1'; NQ <= '0';
  ELSIF S = '0' THEN
    Q <= '0'; NQ <= '1';
  END IF;
END PROCESS;
END ARCHITECTURE;
```

Sequential Statements

Gated-Clock SR Flip-Flop (Latch Enable)

 

ARCHITECTURE Latch_arch OF GC_Latch IS BEGIN
PROCESS (R, S, LE) BEGIN

IF LE='1' THEN

IF R= '0' THEN

Q <= '1'; NQ<='0';

ELSIF S='0' THEN

Q <= '0'; NQ<='1';

END IF;

END IF;

END PROCESS;

END ARCHITECTURE;

Inferring D-Flip Flops: Synchronous

ARCHITECTURE `Dff_arch` OF `Dff` IS
BEGIN

PROCESS (`Clock`) BEGIN
IF `Clock`'EVENT AND `Clock`='1' THEN

`Q` <= `D`;

END IF;
END PROCESS;
END ARCHITECTURE;

Notice the Process
does not contain `D`:
PROCESS(`Clock`, `D`)

Sensitivity lists
contain signals used
in conditionals (i.e. IF)

`Clock`'EVENT is what
distinguishes a D-
FlipFlip from a Latch

Inferring D-Flip Flops: rising_edge



```
ARCHITECTURE Dff_arch OF Dff IS BEGIN
  PROCESS (Clock) BEGIN
    IF Clock'EVENT AND Clock='1' THEN
      Q <= D;
    END IF;
  END PROCESS;
END ARCHITECTURE;
```

Alternate and more readable way is to use the rising_edge function

```
ARCHITECTURE dff_arch OF dff IS BEGIN
  PROCESS (Clock) BEGIN
    IF rising_edge(Clock) THEN
      Q <= D;
    END IF;
  END PROCESS;
END ARCHITECTURE;
```

Inferring D-Flip Flops: Asynchronous Reset



```
ARCHITECTURE dff_reset_arch OF dff_reset IS BEGIN
```

```
    PROCESS (Clock, Reset) BEGIN
```

```
        IF Reset= '1' THEN -- Asynchronous Reset
```

```
            Q <= '0'
```

```
        ELSIF rising_edge(Clock) THEN --Synchronous
```

```
            Q <= D;
```

```
        END IF;
```

```
    END PROCESS;
```

```
END ARCHITECTURE;
```

Inferring D-Flip Flops: Synchronous Reset

```
PROCESS (Clock, Reset) BEGIN
  IF rising_edge(Clock) THEN
    IF Reset='1' THEN
      Q <= '0'
    ELSE
      Q <= D;
    END IF;
  END IF;
END PROCESS;
```

Synchronous Reset
Synchronous FF

```
PROCESS (Clock, Reset) BEGIN
  IF Reset='1' THEN
    Q <= '0'
  ELSIF rising_edge(Clock) THEN
    Q <= D;
  END IF;
END PROCESS;
```


Asynchronous Reset
Synchronous FF

D-Flip Flops: Asynchronous Reset & Preset




```
PROCESS (Clock, Reset, Preset) BEGIN
  IF Reset='1' THEN --highest priority
    Q <= '0';
  ELSIF Preset='1' THEN
    Q <= '0';
  ELSIF rising_edge(Clock) THEN
    Q <= D;
  END IF;
END PROCESS;
```

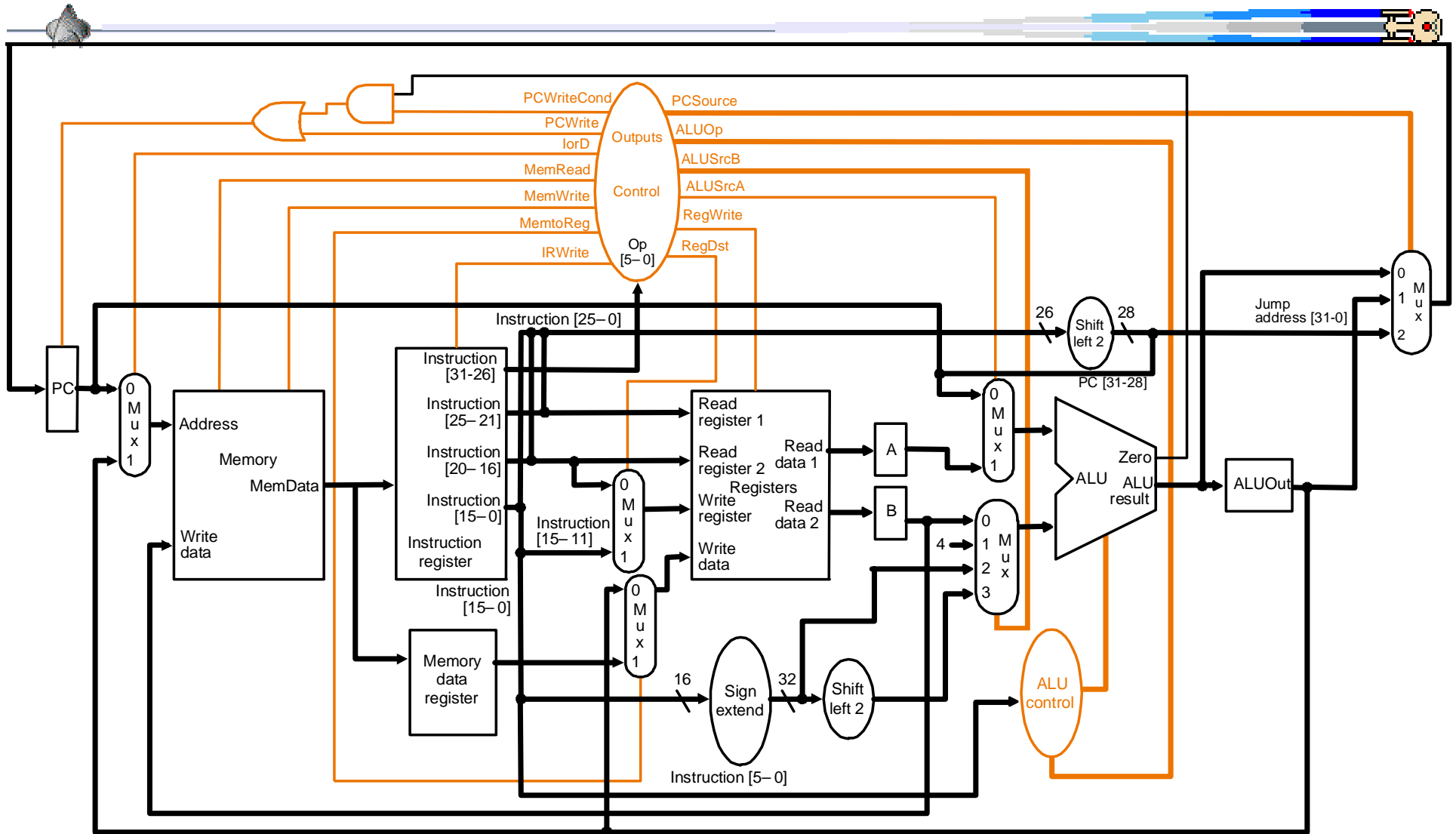RTL Multi-cycle Datapath: with controller



Register Transfer Level (RTL) View

CPU controller: Finite State Machine

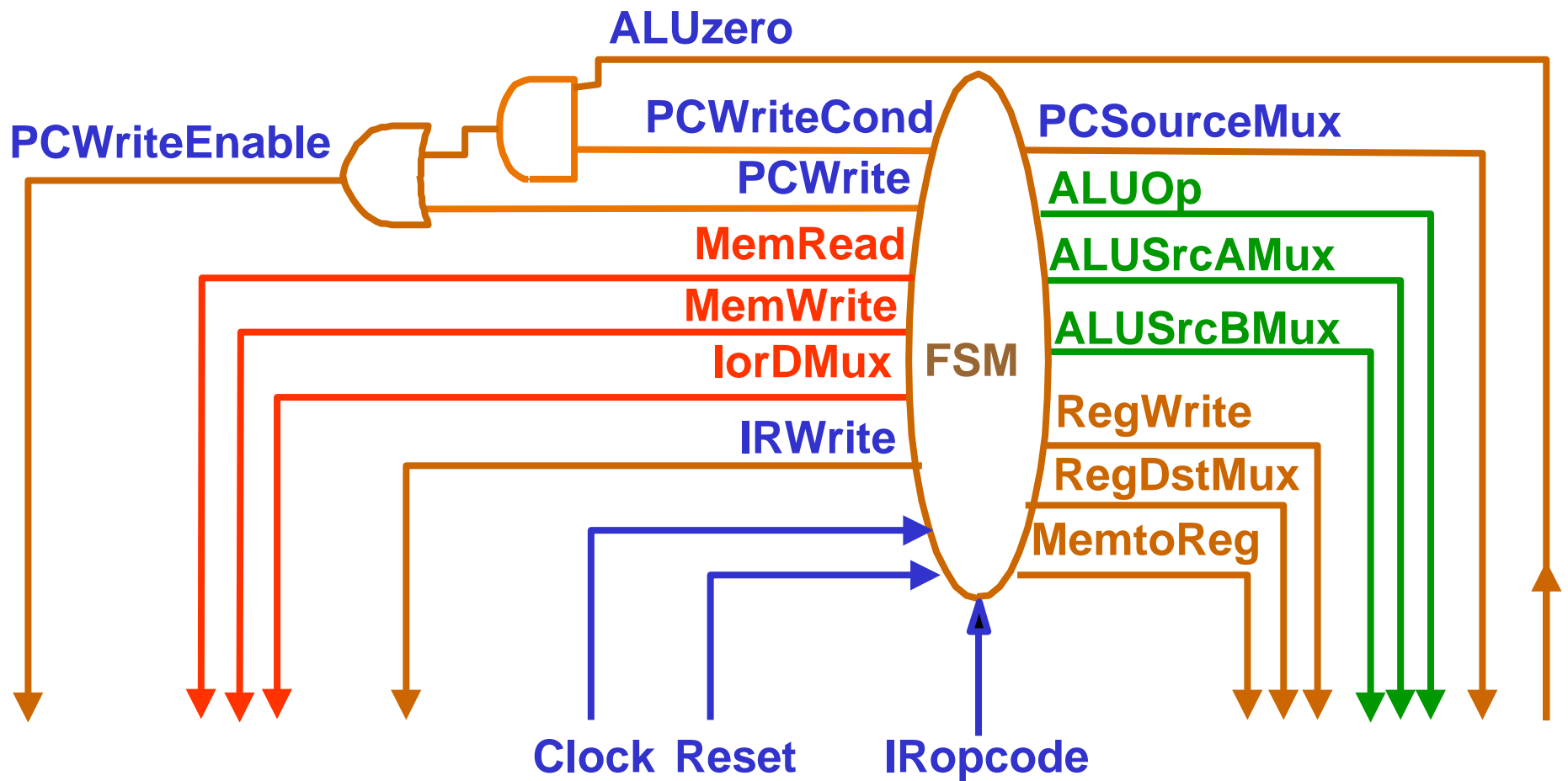


CPU Controller: Entity



```
ENTITY cpu_controller is PORT(  
    CLK, RST           :IN   std_logic;  
    IRopcode           :IN   std_logic_vector(5 downto 0);  
    ALUzero            :IN   std_logic;  
    PCWriteEnable      :OUT  std_logic;  
    PCSourceMux        :OUT  std_logic_vector(1 downto 0);  
    MemRead, MemWrite  :OUT  std_logic;  
    IorDMux            :OUT  std_logic;  
    IRWrite            :OUT  std_logic;  
    RegWrite           :OUT  std_logic;  
    RegDstMux          :OUT  std_logic;  
    MemtoRegMux        :OUT  std_logic;  
    ALUOp              :OUT  std_logic_vector(2 downto 0)  
    ALUSrcAMux         :OUT  std_logic;  
    ALUSrcBMux        :OUT  std_logic_vector(1 downto 0);  
); END ENTITY;
```

CPU controller: R-Format State Machine

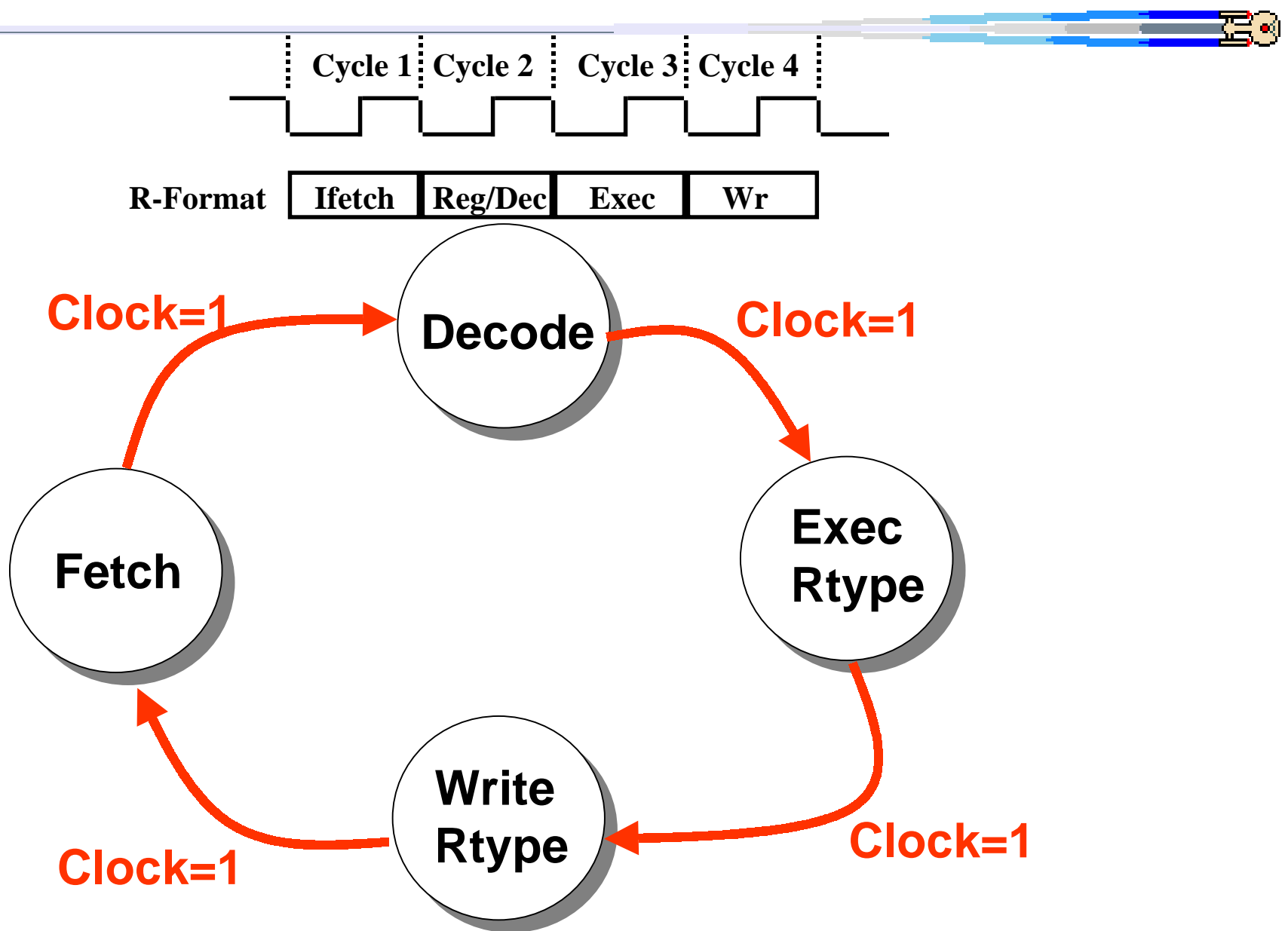

CPU Controller: Current State Process



```
ARCHITECTURE cpu_controller_arch OF cpu_controller IS
  TYPE CPUStates IS (Fetch, Decode, ExecRtype, WriteRtype);
  SIGNAL State, NextState :CPUStates;
BEGIN
```

```
  PROCESS (State) BEGIN
```

```
    CASE State IS
```

```
      WHEN Fetch      => NextState <= Decode;
```

```
      WHEN Decode     => NextState <= ExecRtype;
```

```
      WHEN ExecRtype  => NextState <= WriteRtype;
```

```
      WHEN WriteRtype => NextState <= Fetch;
```

```
      WHEN OTHERS    => NextState <= Fetch;
```

```
    END CASE;
```

```
  END PROCESS;
```

```
  ...
```

CPU controller: NextState Clock Process




```
PROCESS (CLK, RST) BEGIN
  IF RST='1' THEN -- Asynchronous Reset
    State <= Fetch;

    ELSIF rising_edge(CLK) THEN
      State <= NextState;
    END IF;
  END PROCESS;

END ARCHITECTURE;
```

T₁ Fetch: State machine

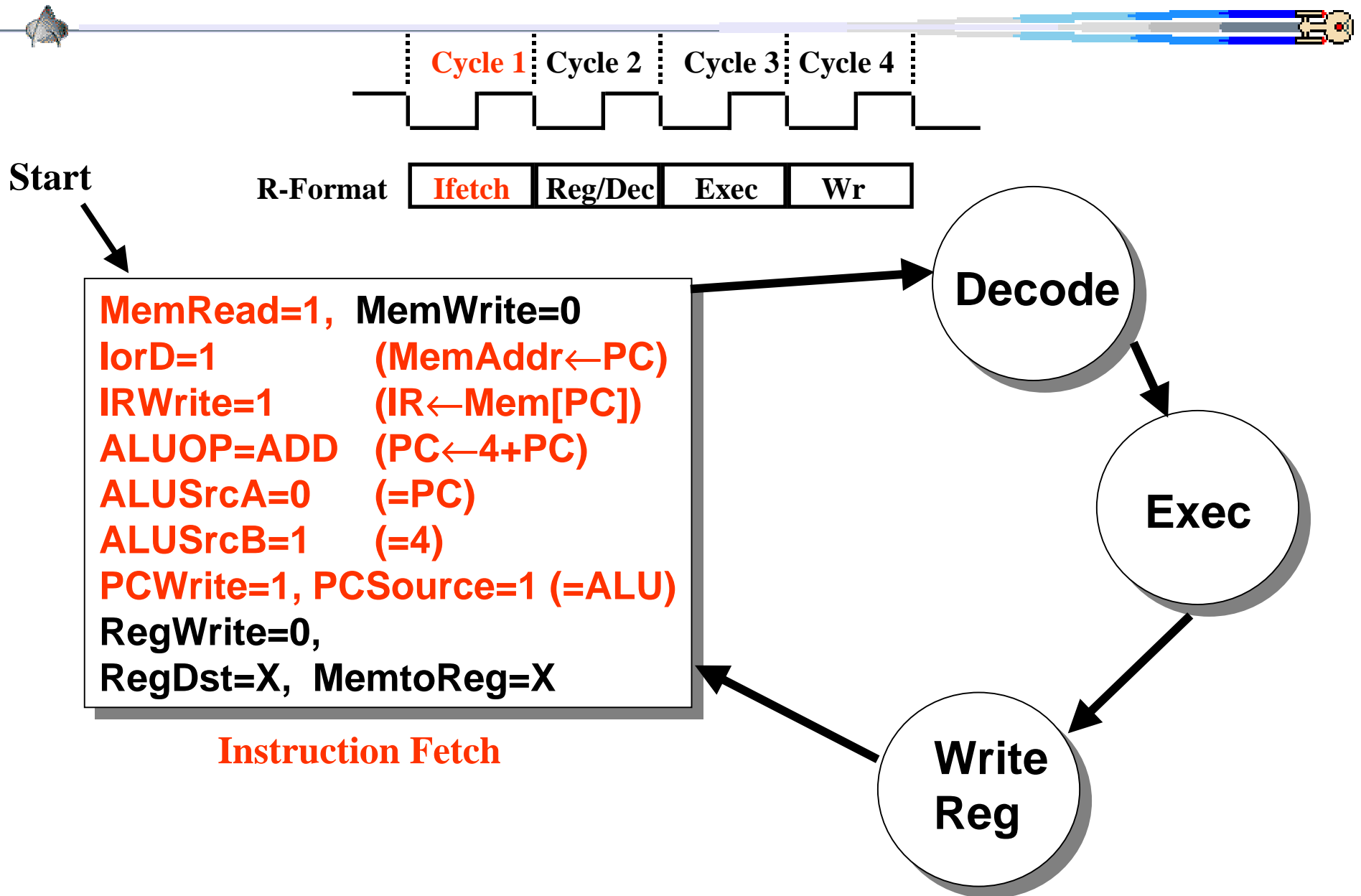

T₁ Fetch: VHDL with Moore Output States

PROCESS (State) BEGIN

CASE State IS

WHEN Fetch =>

NextState <= Decode;

MemRead <= '1';

MemWrite <= '0';

lorD <= '1'

IRWrite <= '1';

ALUOp <= "010"; --add

ALUSrcAMux <= '1'; --PC

ALUSrcBMux <= "01"; --4

PCWriteEnable <= '1';

PCSourceMux <= "00"; --ALU (not ALUOut)

RegWrite <= '0';

RegDstMux <= 'D'; MemtoReg <= 'D';

MemRead=1, MemWrite=0
lorD=1 (MemAddr←PC)
IRWrite=1 (IR←Mem[PC])
ALUOP=ADD (PC←4+PC)
ALUSrcA=0 (=PC)
ALUSrcB=1 (=4)
PCWrite=1, PCSource=1 (=ALU)
RegWrite=0,
RegDst=X, MemtoReg=X

Instruction Fetch

'D' for Don't Care

VHDL inferred Latches: WARNING



In VHDL case statement

The same signal must be defined for each case

Otherwise that signal will be inferred as a latch
and not as combinatorial logic!

For example,

Even though `RegDstMux <= 'D'` is not used
and was removed from the Decode state

This will result in a `RegDstMux`
being inferred as latch not as logic
even though in the `WriteRtype` state it is set

Assignment #3: CPU Architecture design (1/3)



Cyber Dynamics Corporation (18144 El Camino Real, S'Vale California) needs the following embedded model 101 microprocessor designed by *Thursday October 5, 2000* with the following specifications

- 16 bit instruction memory using ROM
 - 8 bit data memory using RAM
 - There are eight 8-bit registers
 - The instruction set is as follows
-
- All Arithmetic and logical instructions set a Zero one-bit flag (Z) based on ALU result
 - add, adc, sub, sbc set the Carry/Borrow one-bit Flag (C) based on ALU result

Assignment #3: CPU Architecture design (2/3)



Arithmetic and logical instructions

add \$rt,\$rs	#\$rt = \$rt +\$rs; C=ALUcarry; Z=\$rt
adc \$rt, \$rs	#\$rt = \$rt +\$rs+C; C=ALUcarry; Z;
sub \$rt, \$rs	#\$rt = \$rt - \$rs; C=ALUborrow; Z;
sub \$rt, \$rs	#\$rt = \$rt - \$rs - borrow; C; Z;
and \$rt, \$rs	#\$rt = \$rt & \$rs; C=0; Z=\$rt;
or \$rt, \$rs	#\$rt = \$rt \$rs; C=0; Z=\$rt;
xor \$rt, \$rs	#\$rt = \$rt ^ \$rs; C=1; Z=\$rt;

Other Instructions continued):

lbi	\$r, immed	#\$r = immediate
lbr	\$rt,\$rs	#\$rt = Mem[\$rs]
lb	\$r, address	#\$r = Mem[address]
stb	\$r, address	#Mem[address]=\$r
bz	address	#if zero then pc=pc+2+addr
bc	address	#if carry then pc=pc+2+addr
j	address	#pc = address
jr	\$r	#pc = \$r

Assignment #3: CPU Architecture design (2/3)



- (1a) Design an RTL diagram of the model 101 processor and**
- (1b) Opcode formats and**
- (1c) Opcode bits of a Harvard Architecture CPU (determine your own field sizes).**
- (1d) What is the size of the Program Counter?**
- (2) Write the assembly code for a 32 bit add $Z=X+Y$ located in memory address for $@X = 0x80$ $@Y = 0x84$ and $@Z=0x88$**
- (3) Draw the state diagram for your FSM controller**
- (4) Write the VHDL code for the FSM controller**

Note: this will be part of your final project report